

# Computer Architecture

## Lec 4b: Multi-Cycle Datapath

# Multi-Cycle Microarchitectures

# Multi-Cycle Microarchitectures

---

- Goal: Let each instruction take (close to) only as much time it really needs
- Idea
  - Determine clock cycle time independently of instruction processing time
  - Each instruction takes as many clock cycles as it needs to take
    - Multiple state transitions per instruction
    - The states followed by each instruction is different


# Multi-Cycle Microarchitectures

---

- Key Idea for Realization
  - One can implement the “process instruction” step as a **finite state machine** that sequences between states and eventually returns back to the “fetch instruction” state
  - A state is defined by the control signals asserted in it
  - Control signals for the next state are determined in current state

# The Instruction Processing Cycle

---

 


# A Basic Multi-Cycle Microarchitecture

---

- Instruction processing cycle divided into “states”
  - A stage in the instruction processing cycle can take multiple states
- A multi-cycle microarchitecture sequences from state to state to process an instruction
  - The behavior of the machine in a state is completely determined by control signals in that state
- The behavior of the entire processor is specified fully by a *finite state machine*
- In a state (clock cycle), control signals control two things:
  - How the datapath should process the data
  - How to generate the control signals for the (next) clock cycle

# Remember: Single-Cycle MIPS Processor

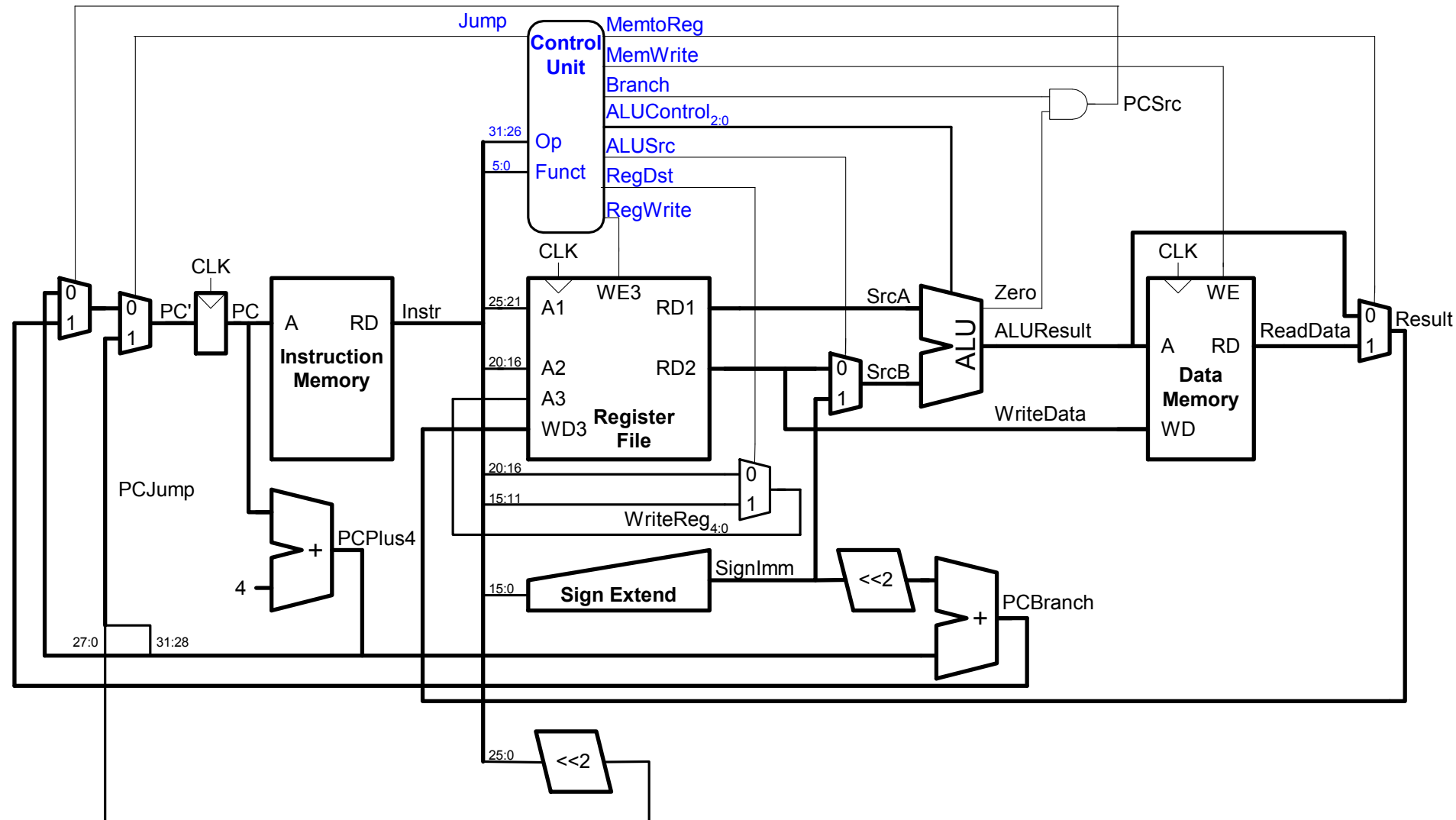

# Multi-cycle MIPS Processor

---

- Single-cycle microarchitecture:
  - cycle time limited by longest instruction (1w) → low clock frequency
  - three adders/ALUs and two memories → high hardware cost
- Multi-cycle microarchitecture:
  - + higher clock frequency
  - + simpler instructions run faster
  - + reuse expensive hardware across multiple cycles
  - sequencing overhead paid many times
  - hardware overhead for storing intermediate results
- Same design steps: datapath & control



# What Do We Want To Optimize

---

- Single Cycle Architecture uses two memories
  - One memory stores instructions, the other data
  - We want to use a single memory (Smaller size)

# What Do We Want To Optimize

---

- Single Cycle Architecture uses two memories
  - One memory stores instructions, the other data
  - We want to use a single memory (Smaller size)
- Single Cycle Architecture needs three adders
  - ALU, PC, Branch address calculation
  - We want to use the ALU for all operations (smaller size)

# What Do We Want To Optimize

---

- Single Cycle Architecture uses two memories
  - One memory stores instructions, the other data
  - We want to use a single memory (Smaller size)
- Single Cycle Architecture needs three adders
  - ALU, PC, Branch address calculation
  - We want to use the ALU for all operations (smaller size)
- In Single Cycle Architecture all instructions take one cycle
  - The most complex operation slows down everything!
  - Divide all instructions into multiple steps
  - Simpler instructions can take fewer cycles (average case may be faster)

# Consider the `lw` instruction


---

- For an instruction such as: `lw $t0, 0x20($t1)`
- We need to:
  - Read the instruction from memory
  - Then read `$t1` from register array
  - Add the immediate value (`0x20`) to calculate the memory address
  - Read the content of this address
  - Write to the register `$t0` this content

# Multi-cycle Datapath: instruction fetch

## ■ First consider executing lw

### ■ STEP 1: Fetch instruction

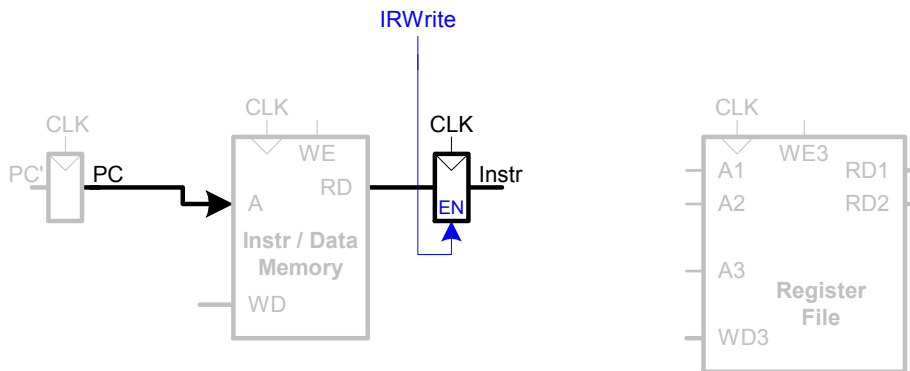


read from the memory location  $[rs] + imm$  to location  $[rt]$

### I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits


# Multi-cycle Datapath: lw register read

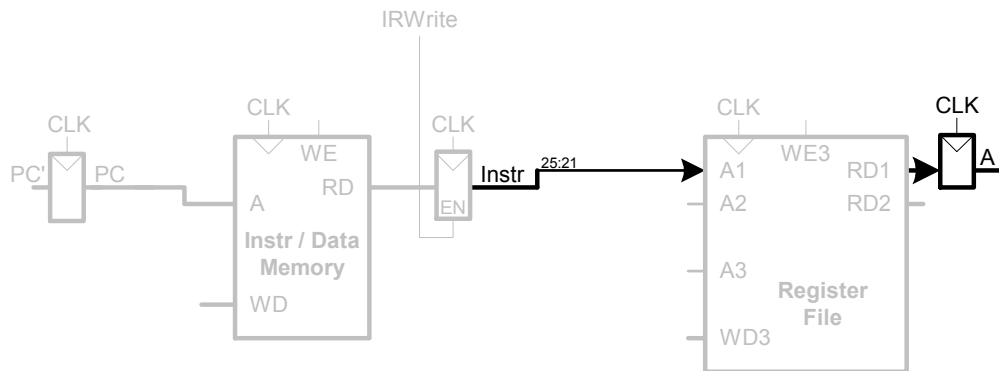

## I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits


# Multi-cycle Datapath: 1w immediate

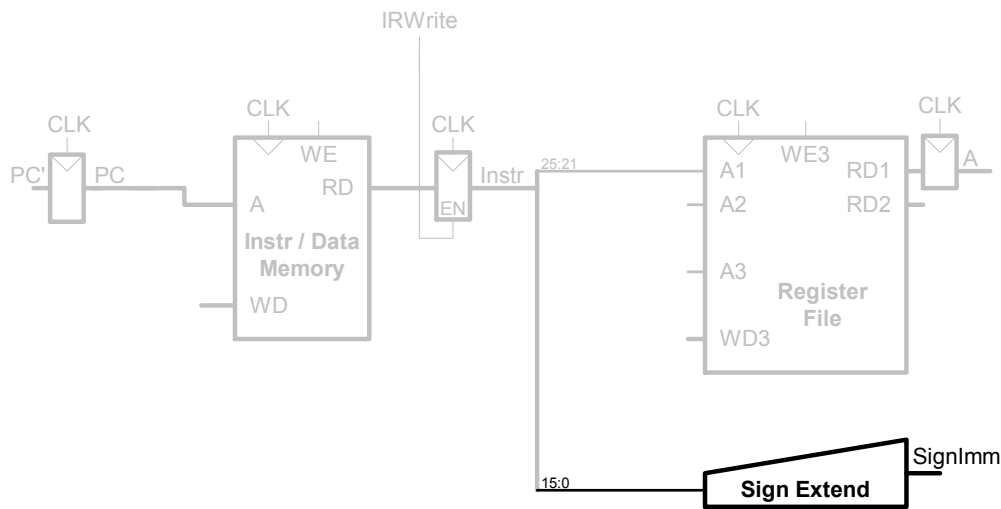

## I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

# Multi-cycle Datapath: 1w address

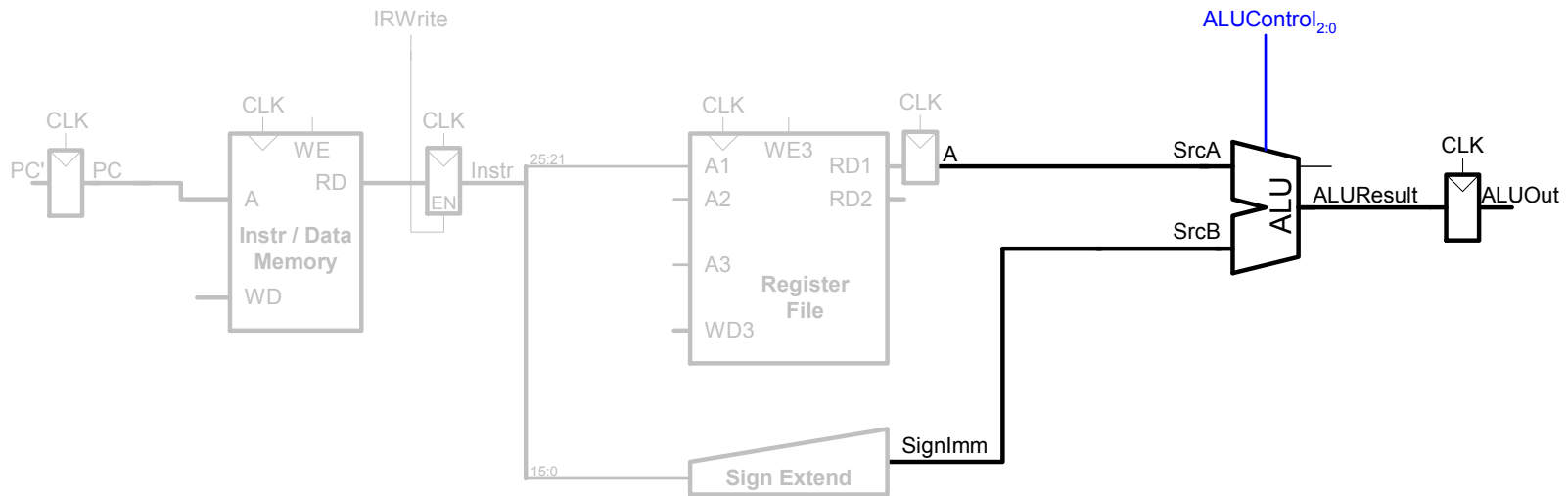


## I-Type





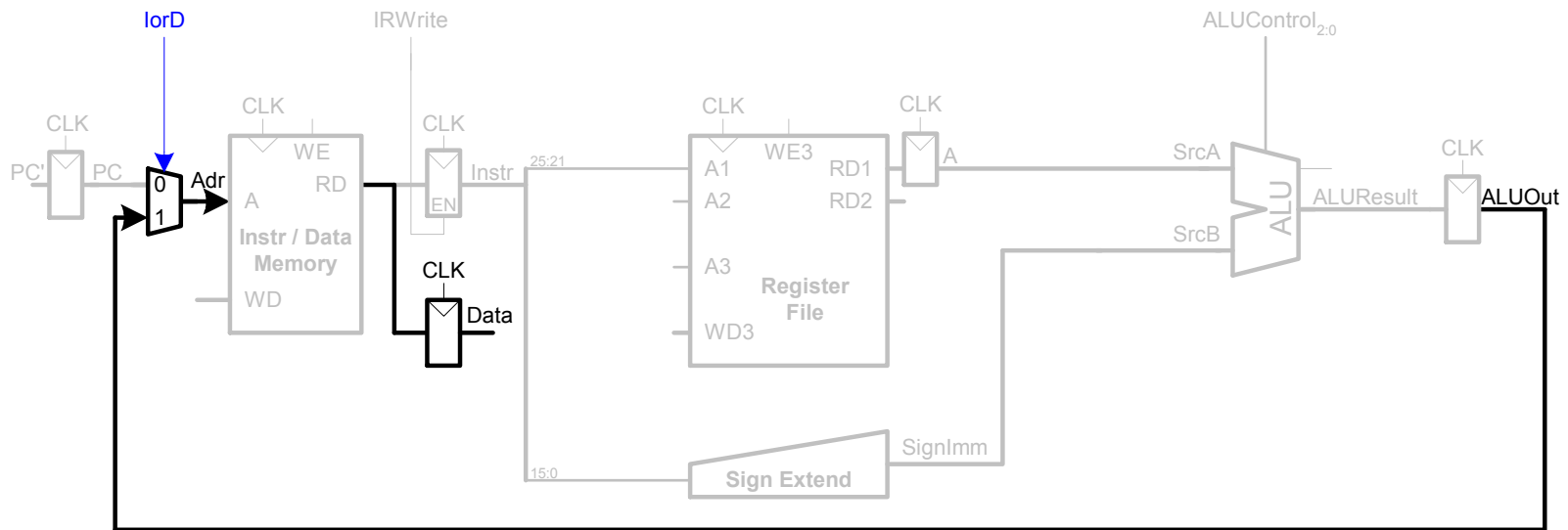
# Multi-cycle Datapath: **lw** memory read



## **I-Type**

<b>op</b>	<b>rs</b>	<b>rt</b>	<b>imm</b>
6 bits	5 bits	5 bits	16 bits

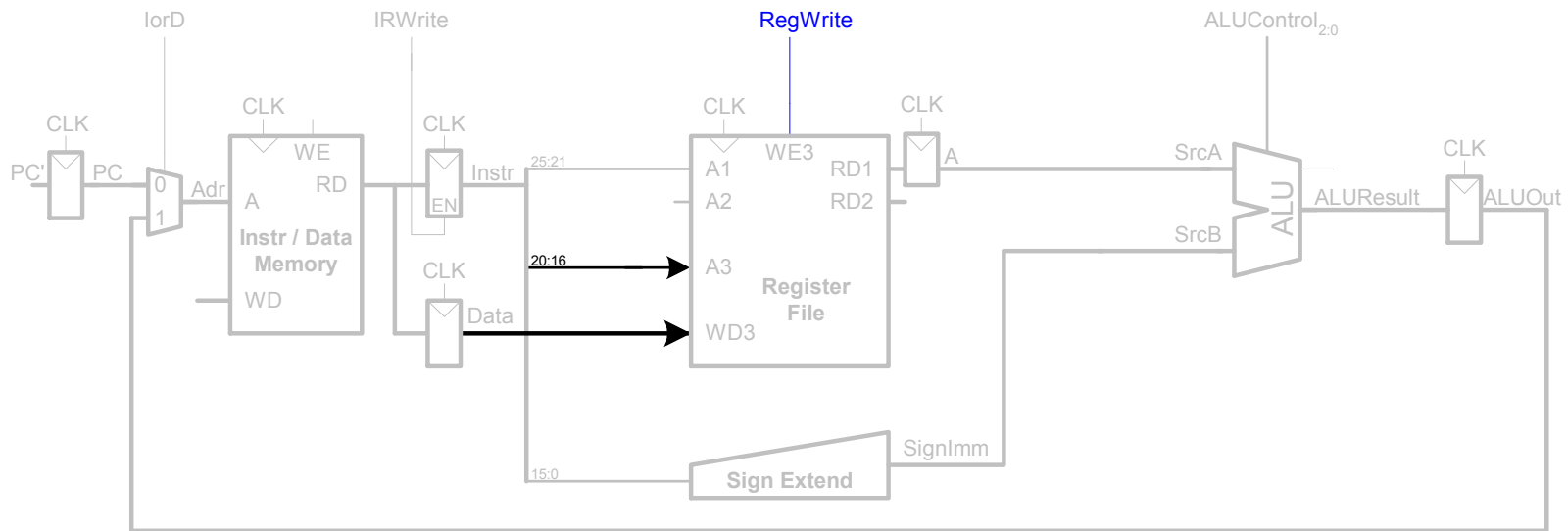
# Multi-cycle Datapath: 1w write register



## I-Type


op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

# Multi-cycle Datapath: increment PC

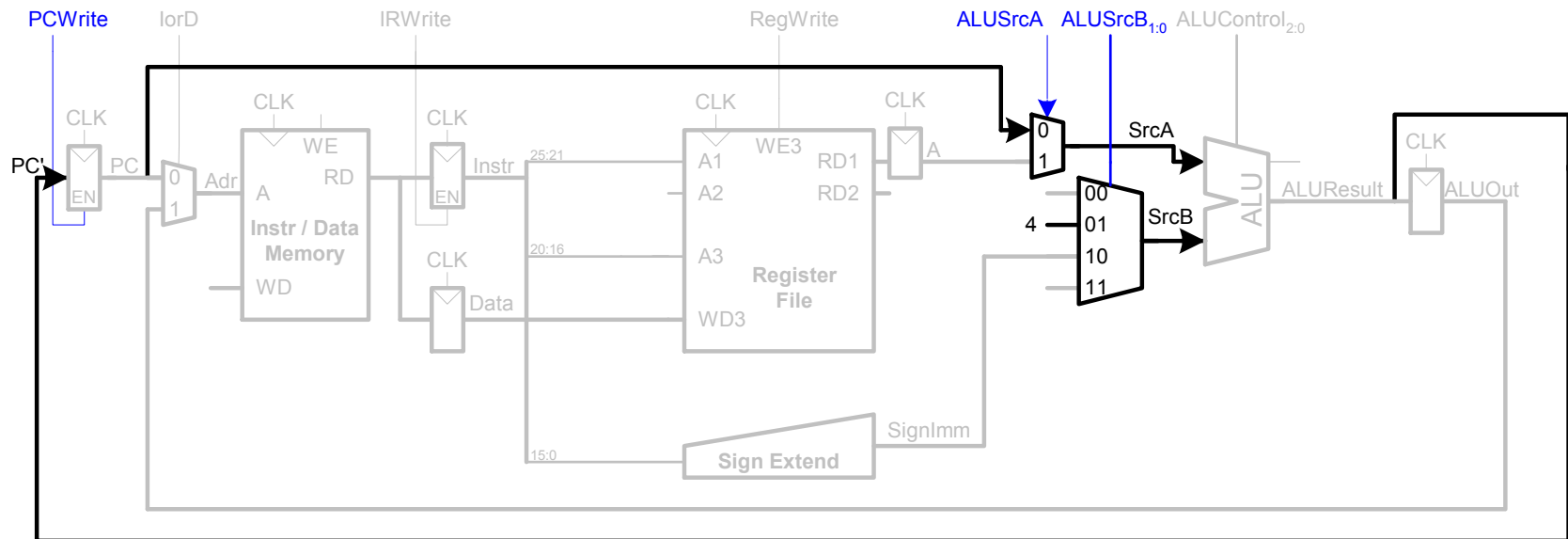

# Multi-cycle Datapath: sw


## ■ Write data in rt to memory

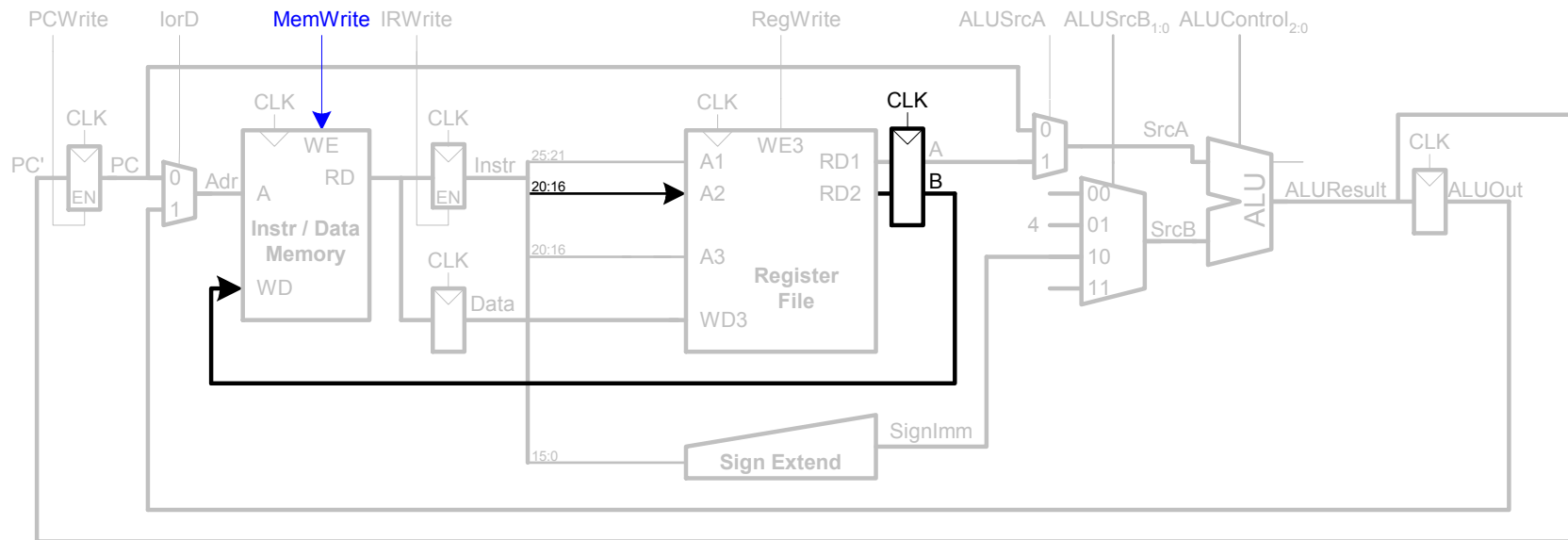

# Multi-cycle Datapath: R-type Instructions
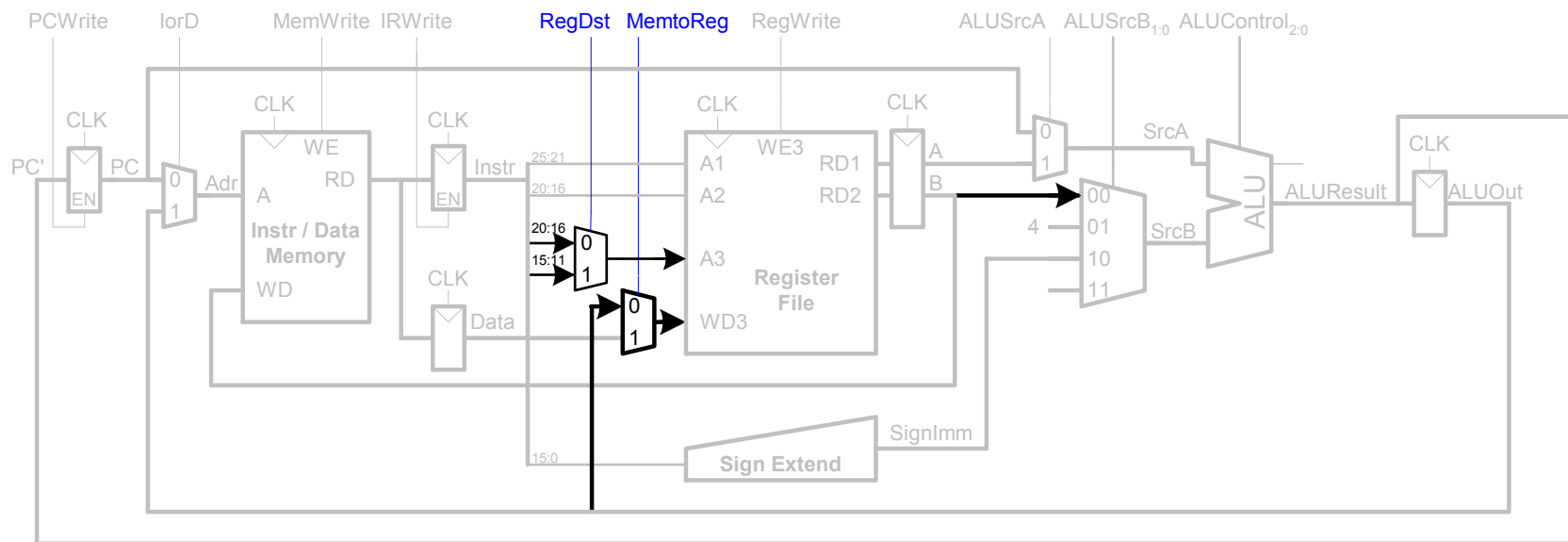
## ■ Read from rs and rt

- Write ALUResult to register file
- Write to rd (instead of rt)




# Multi-cycle Datapath: beq


- Determine whether values in rs and rt are equal

- Calculate branch target address:

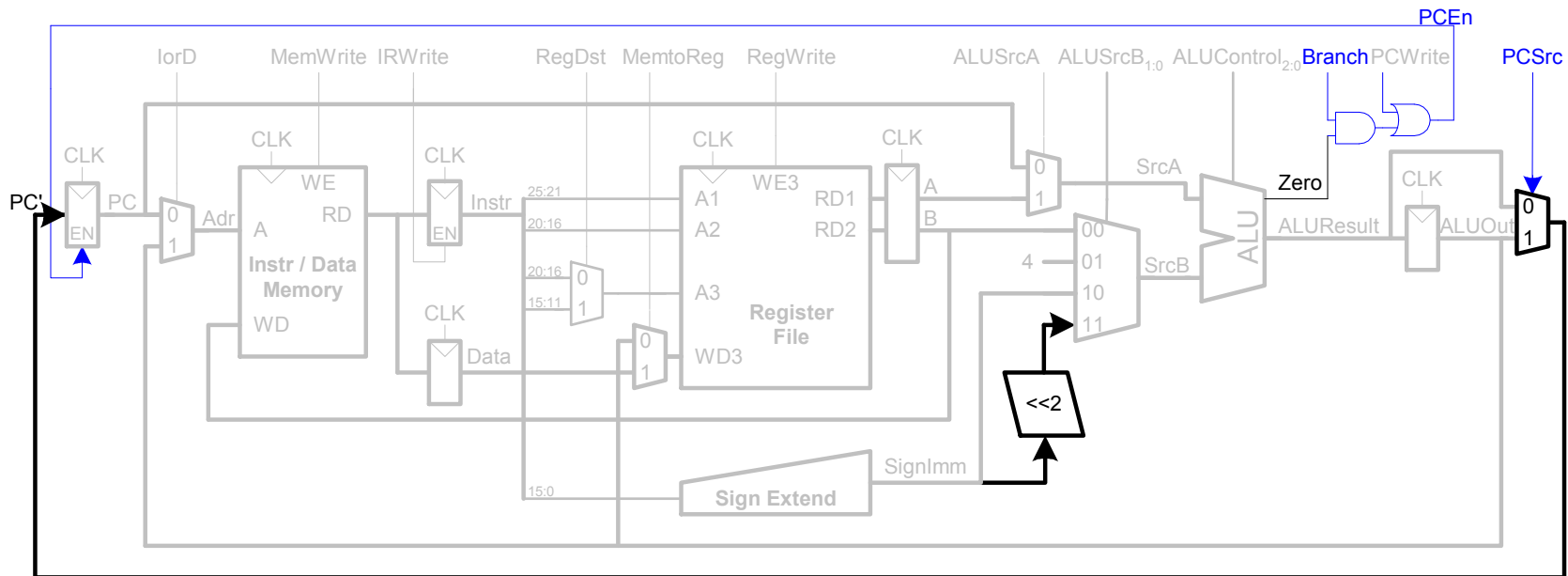
**BTA** = (sign-extended immediate << 2) + (PC+4)



# Complete Multi-cycle Processor


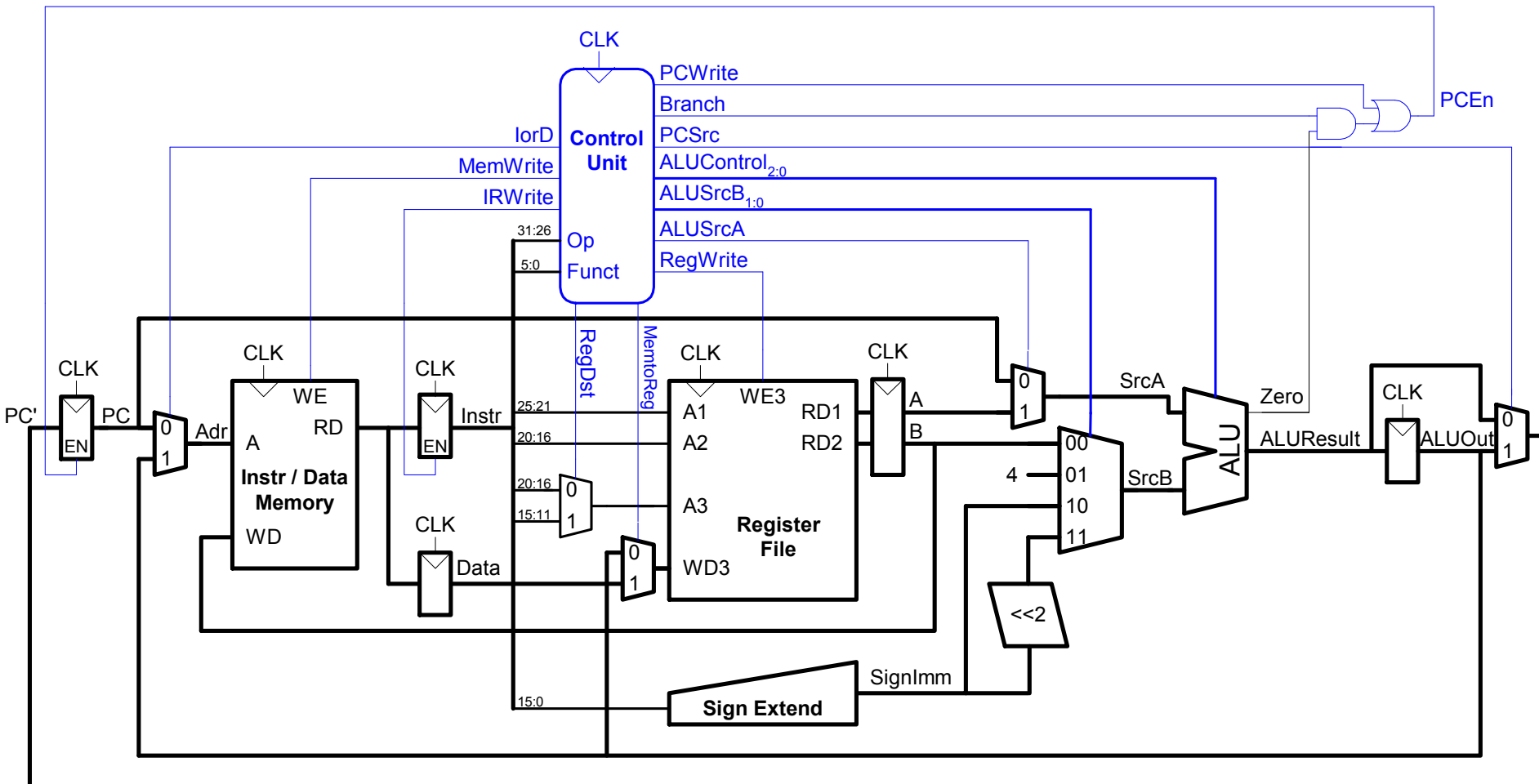


# Control Unit

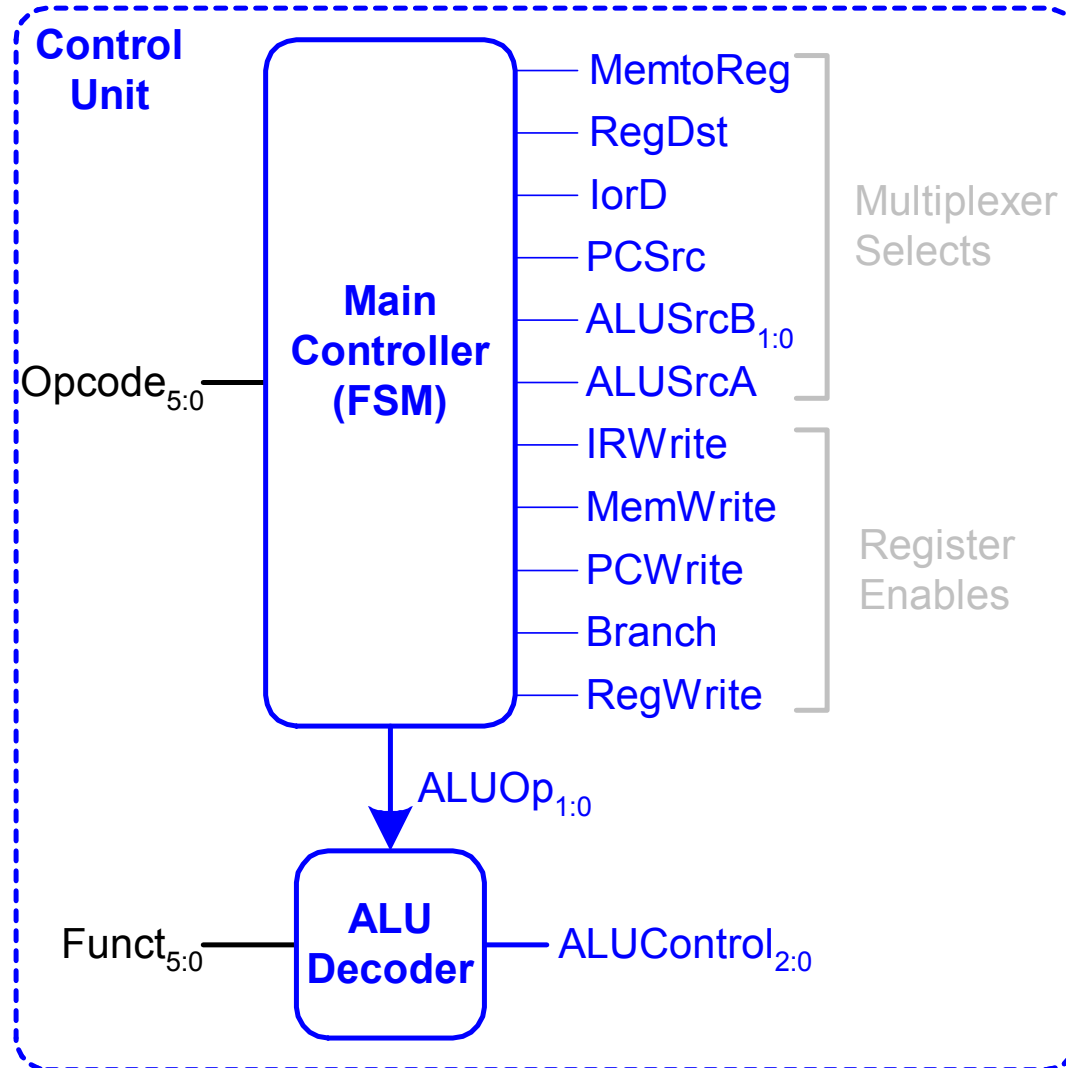



# Main Controller FSM: Fetch

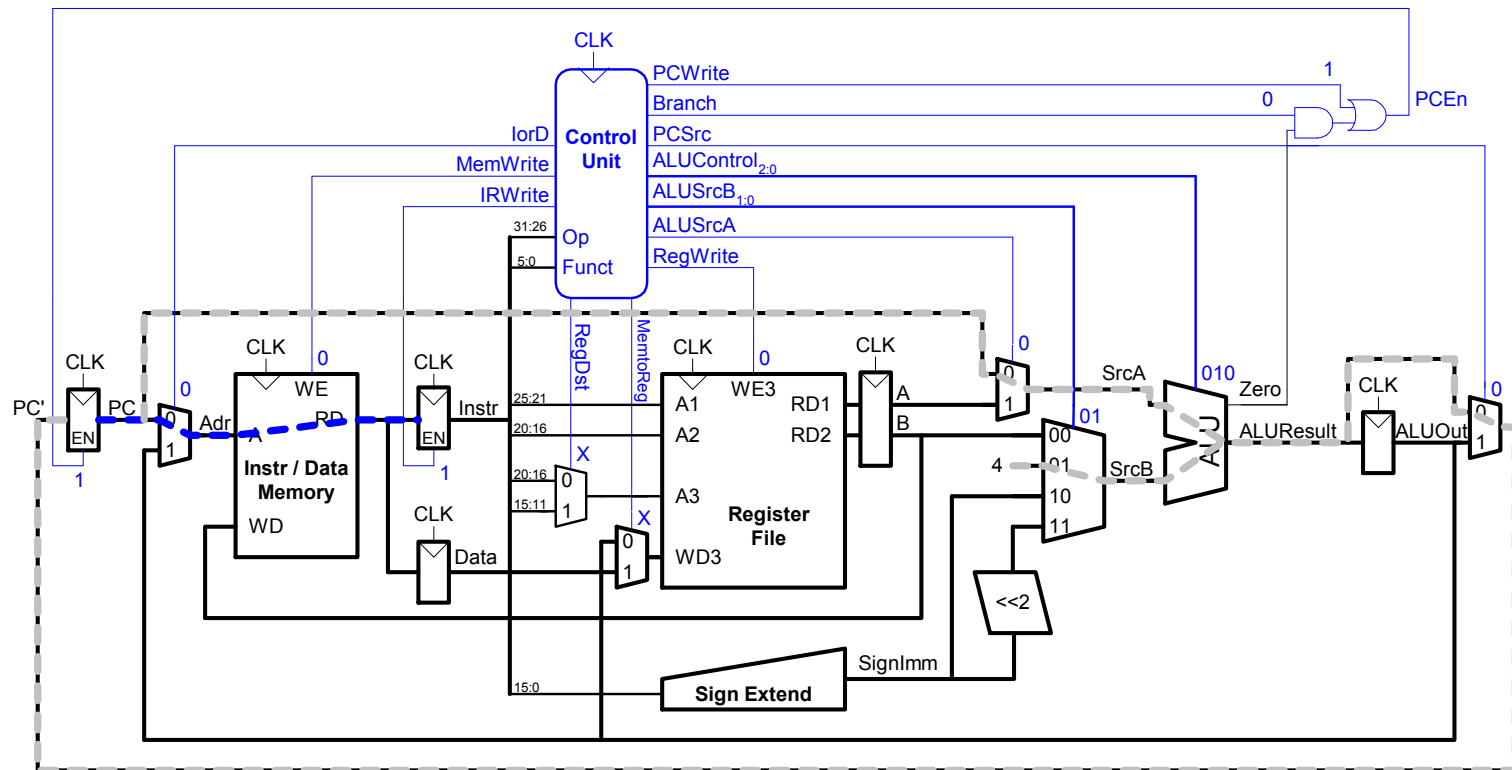 


# Main Controller FSM: Fetch

S0: Fetch

Reset

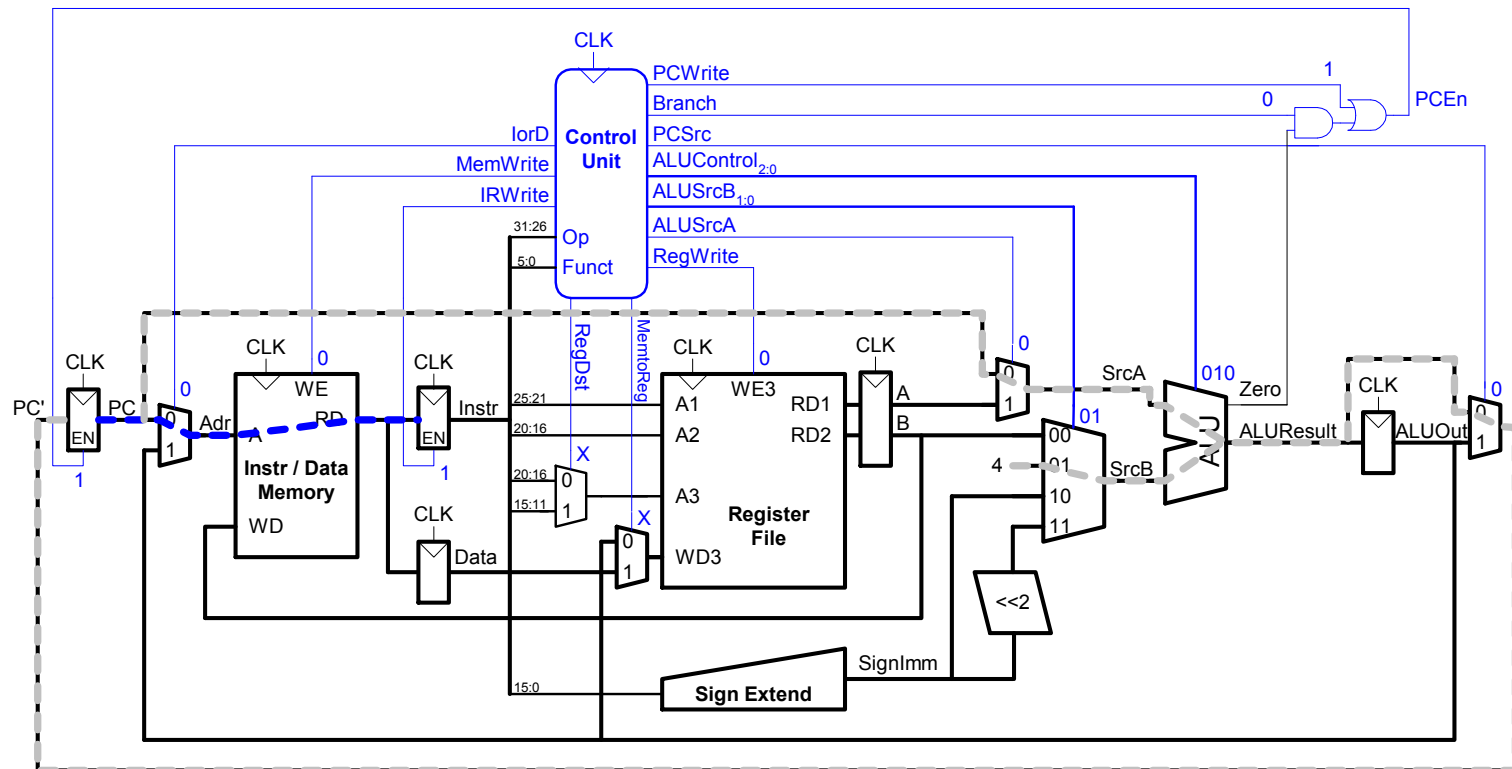lorD = 0  
AluSrcA = 0  
ALUSrcB = 01  
ALUOp = 00  
PCSrc = 0  
IRWrite  
PCWrite




# Main Controller FSM: Decode

S0: Fetch


S1: Decode

Reset

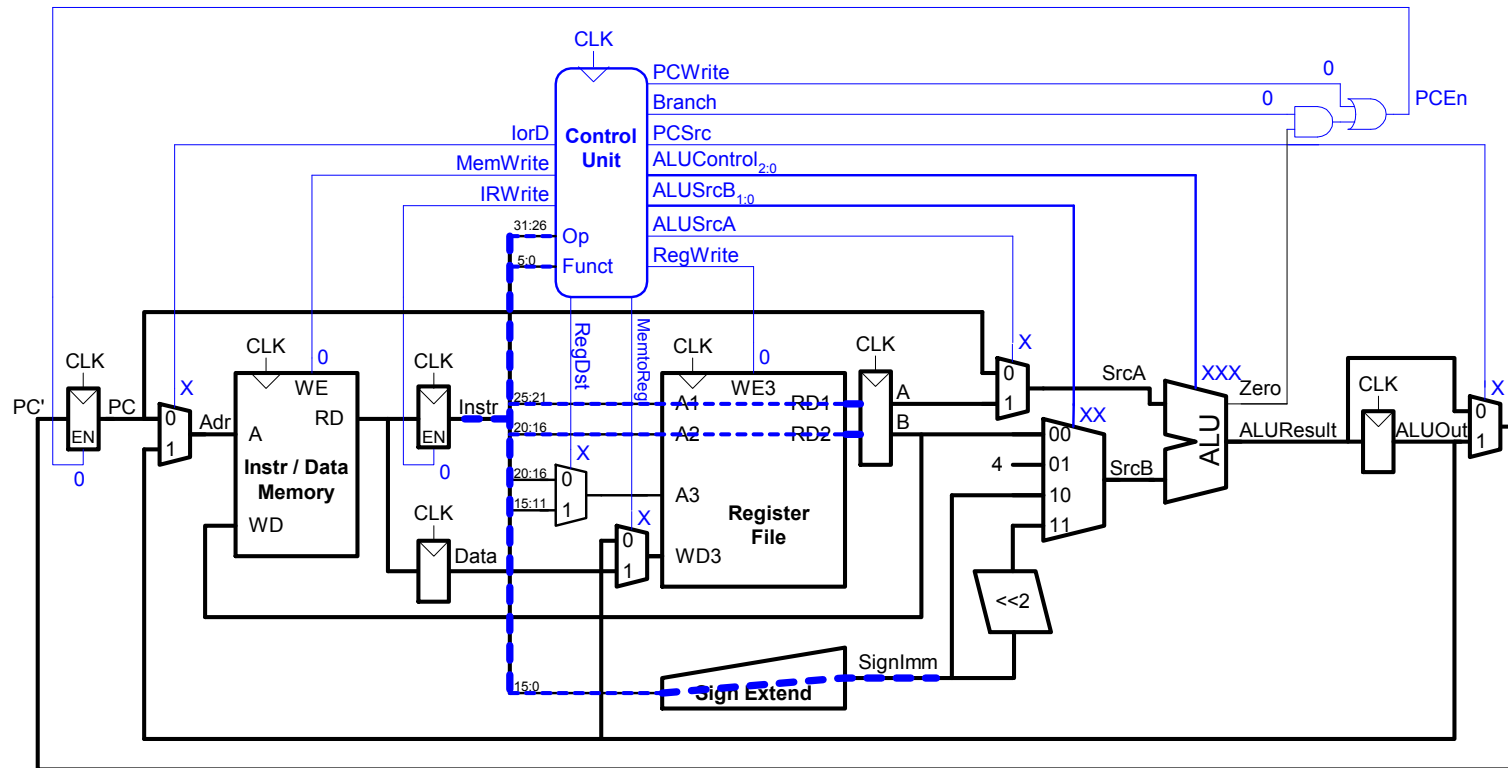
lorD = 0  
AluSrcA = 0  
ALUSrcB = 01  
ALUOp = 00  
PCSrc = 0  
IRWrite  
PCWrite



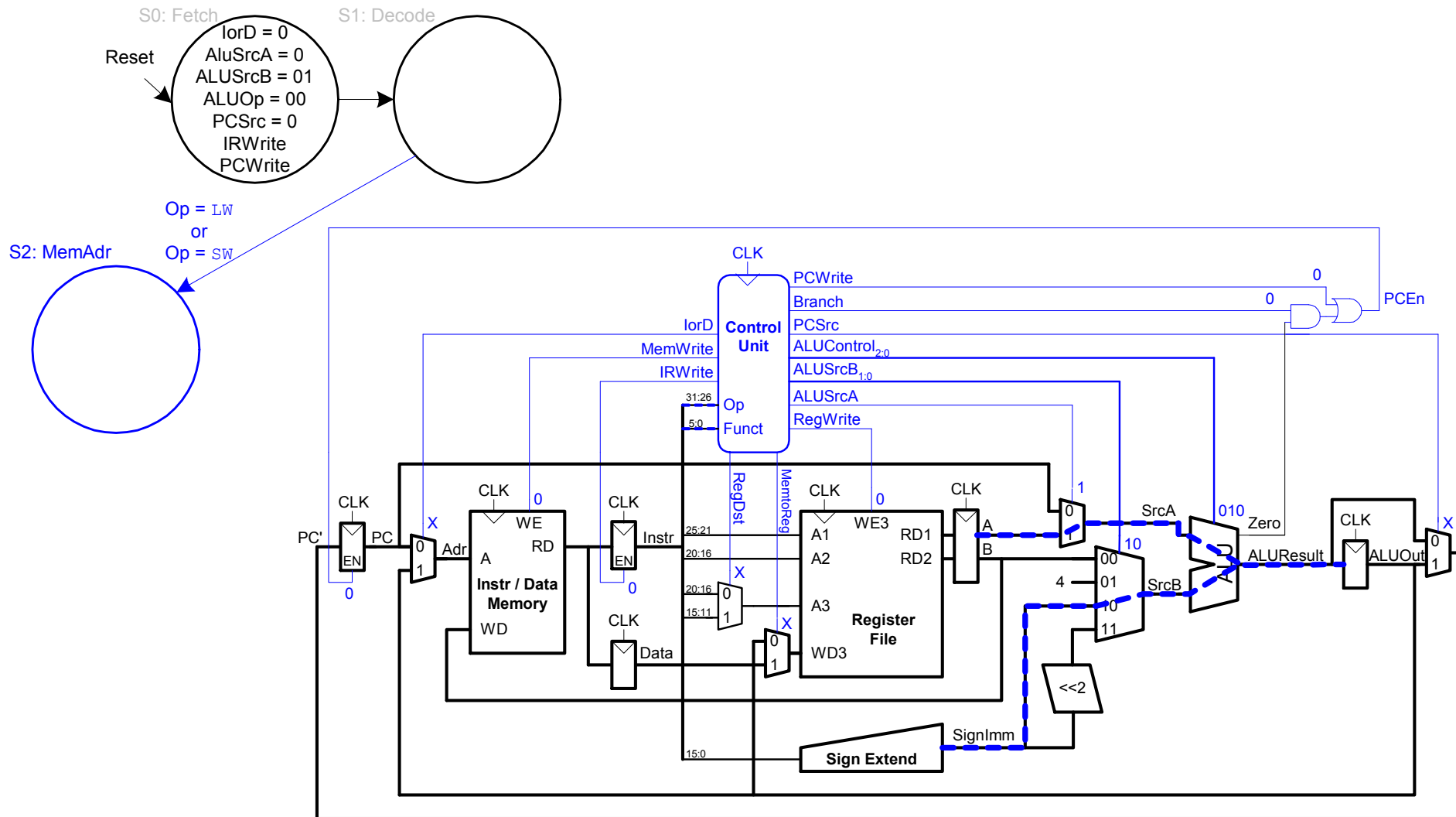
# Main Controller FSM: Address Calculation



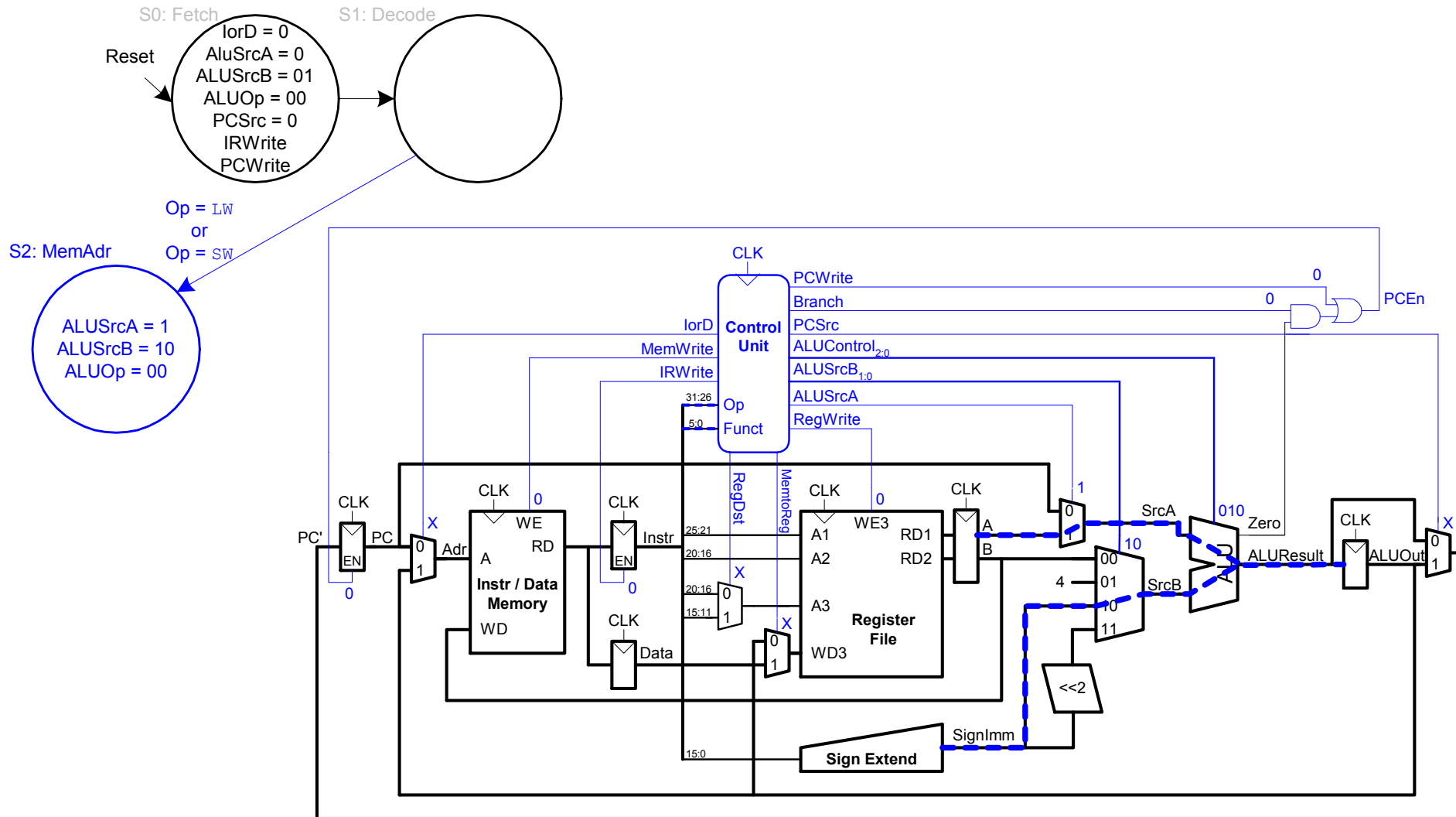
# Main Controller FSM: Address Calculation




# Main Controller FSM: lw

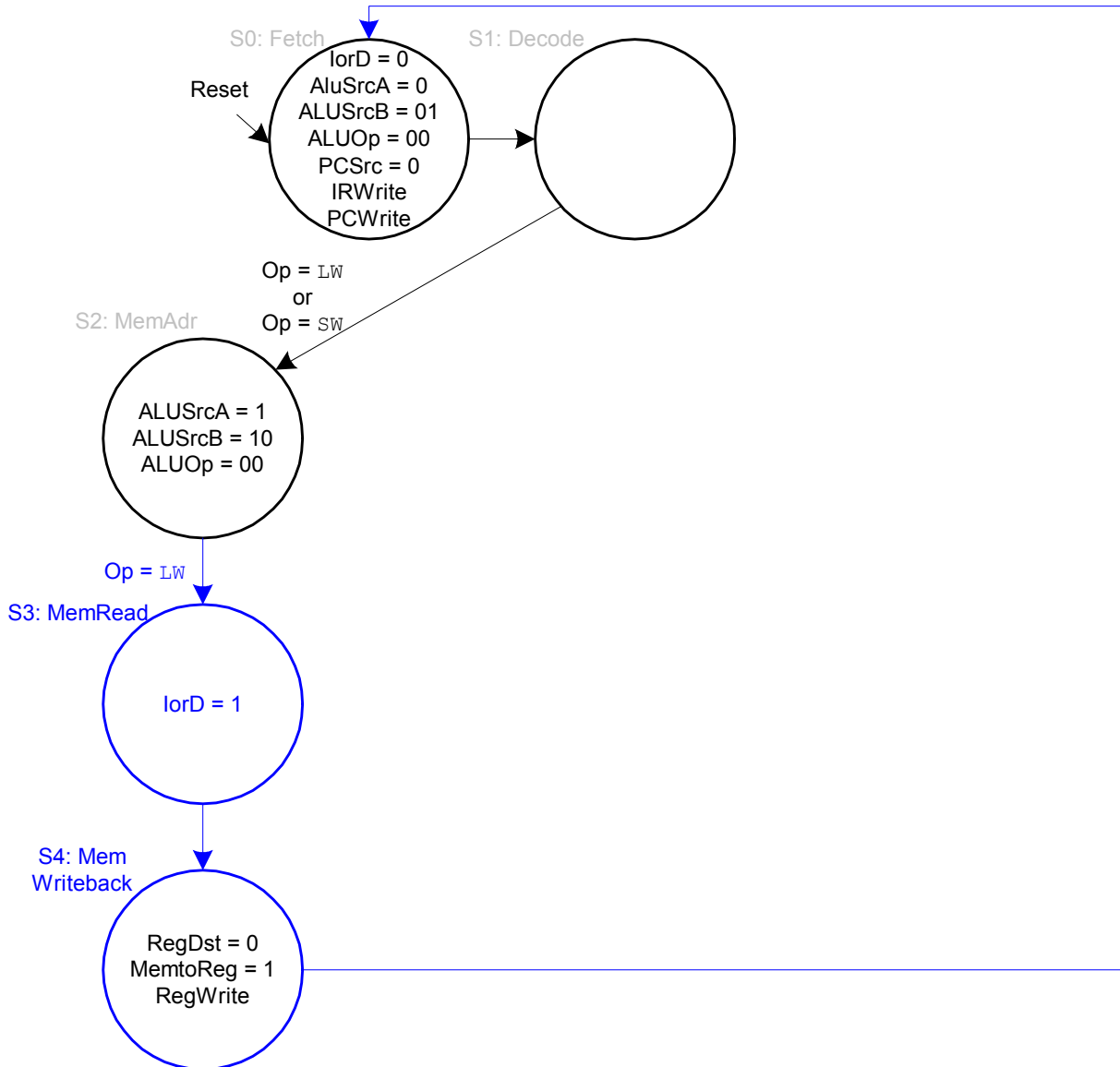

# Main Controller FSM: sw

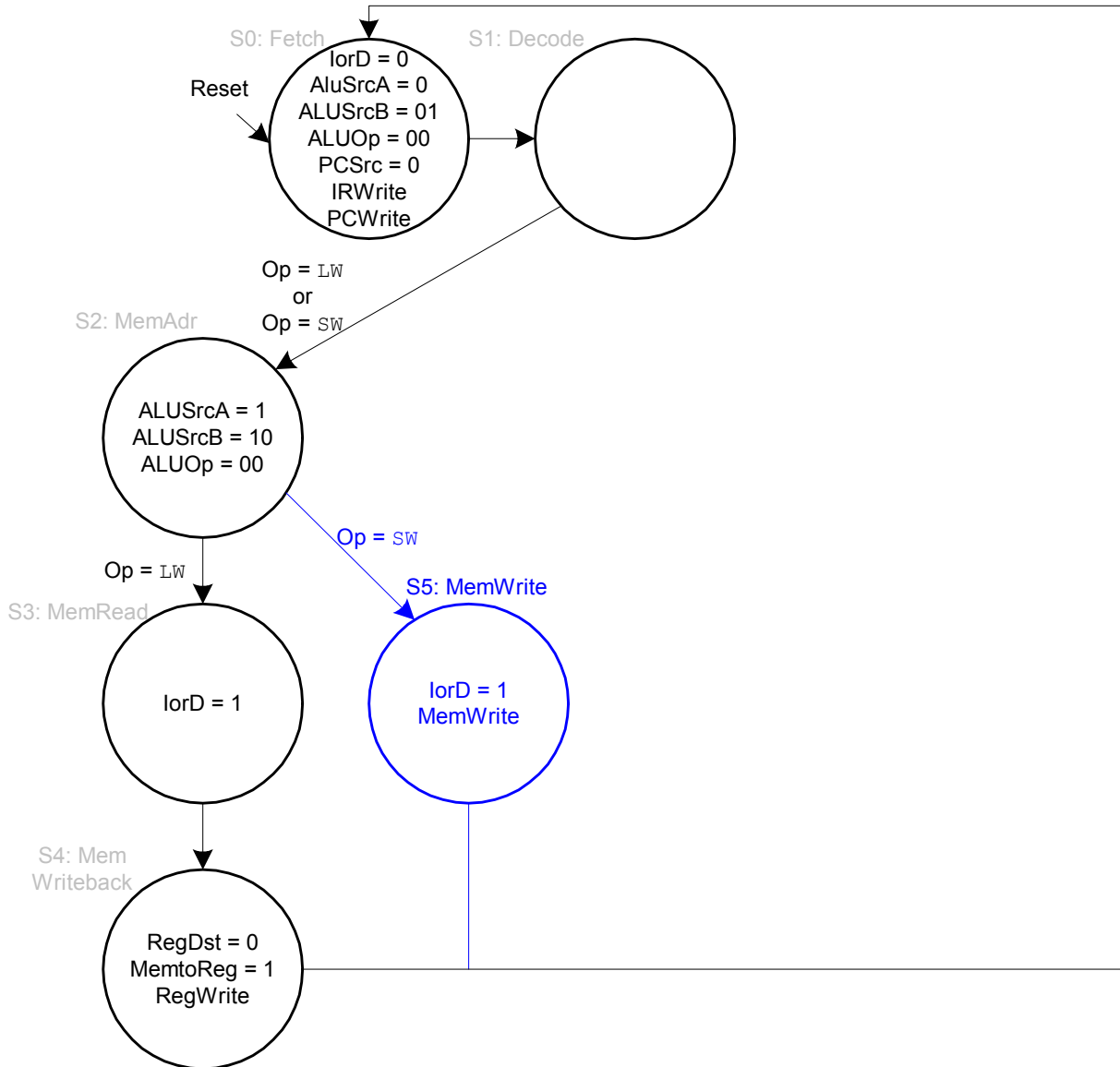


# Main Controller FSM: R-Type

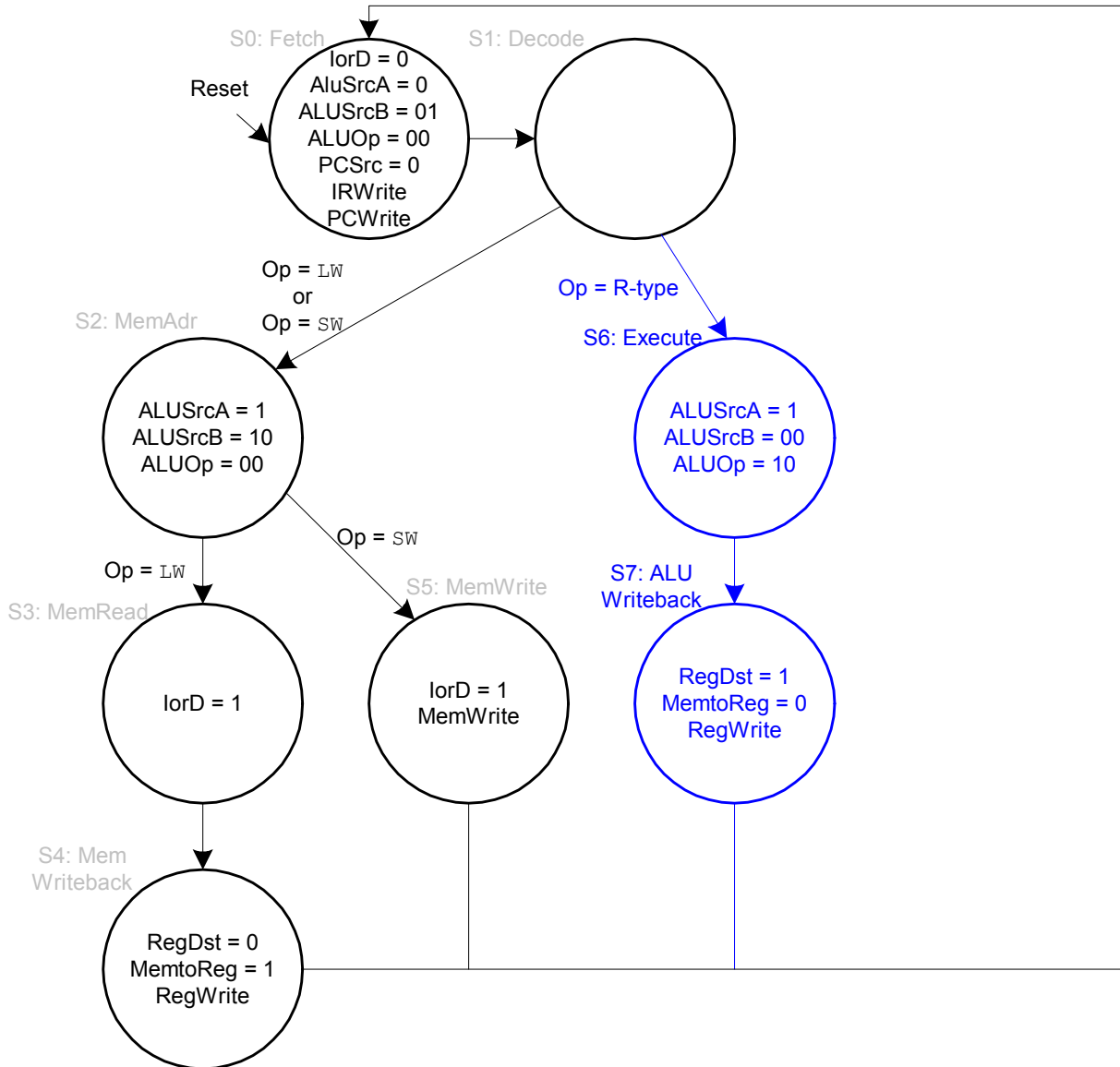





# Main Controller FSM: beq

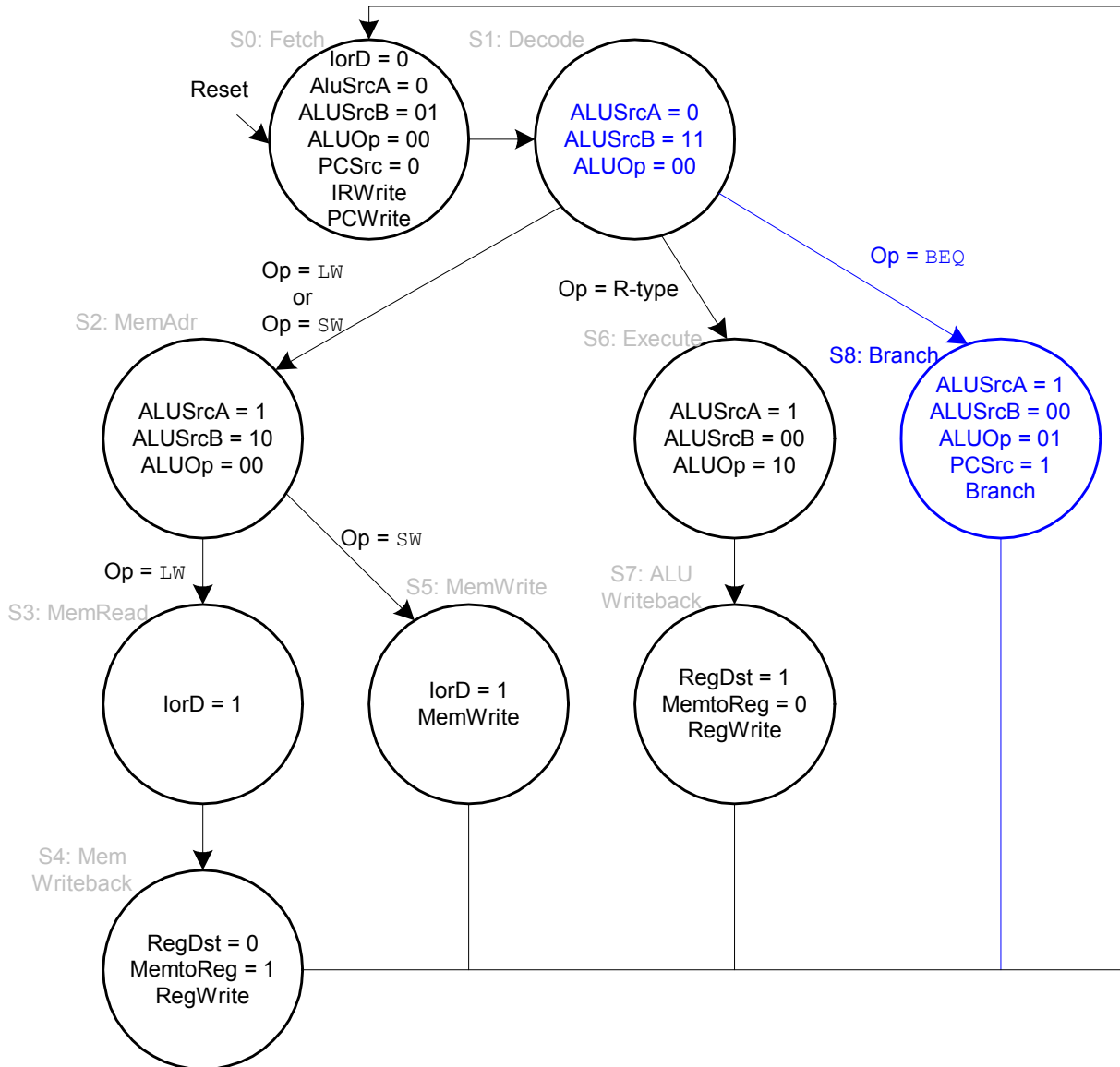


# Complete Multi-cycle Controller FSM

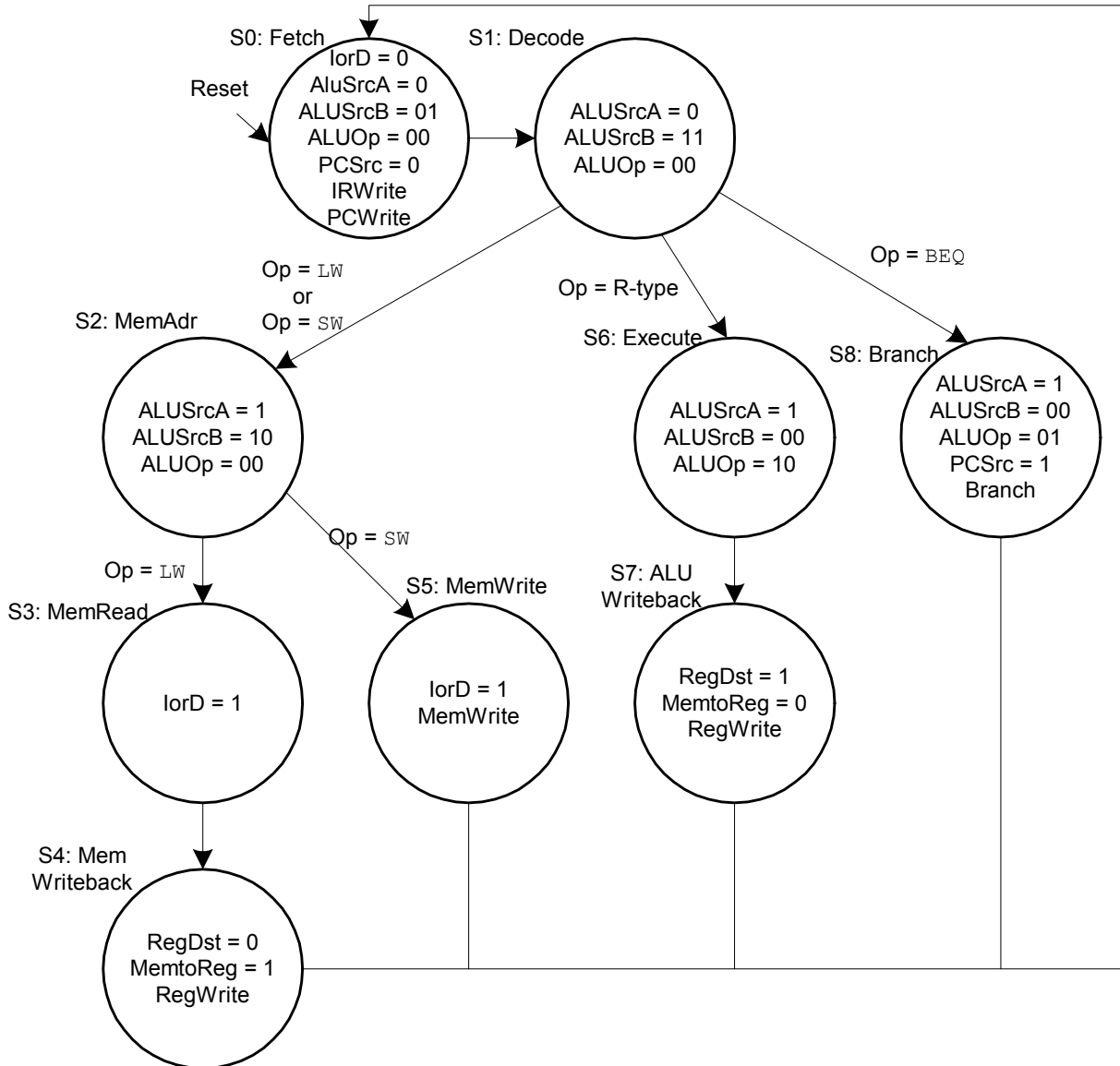


# Main Controller FSM: addi

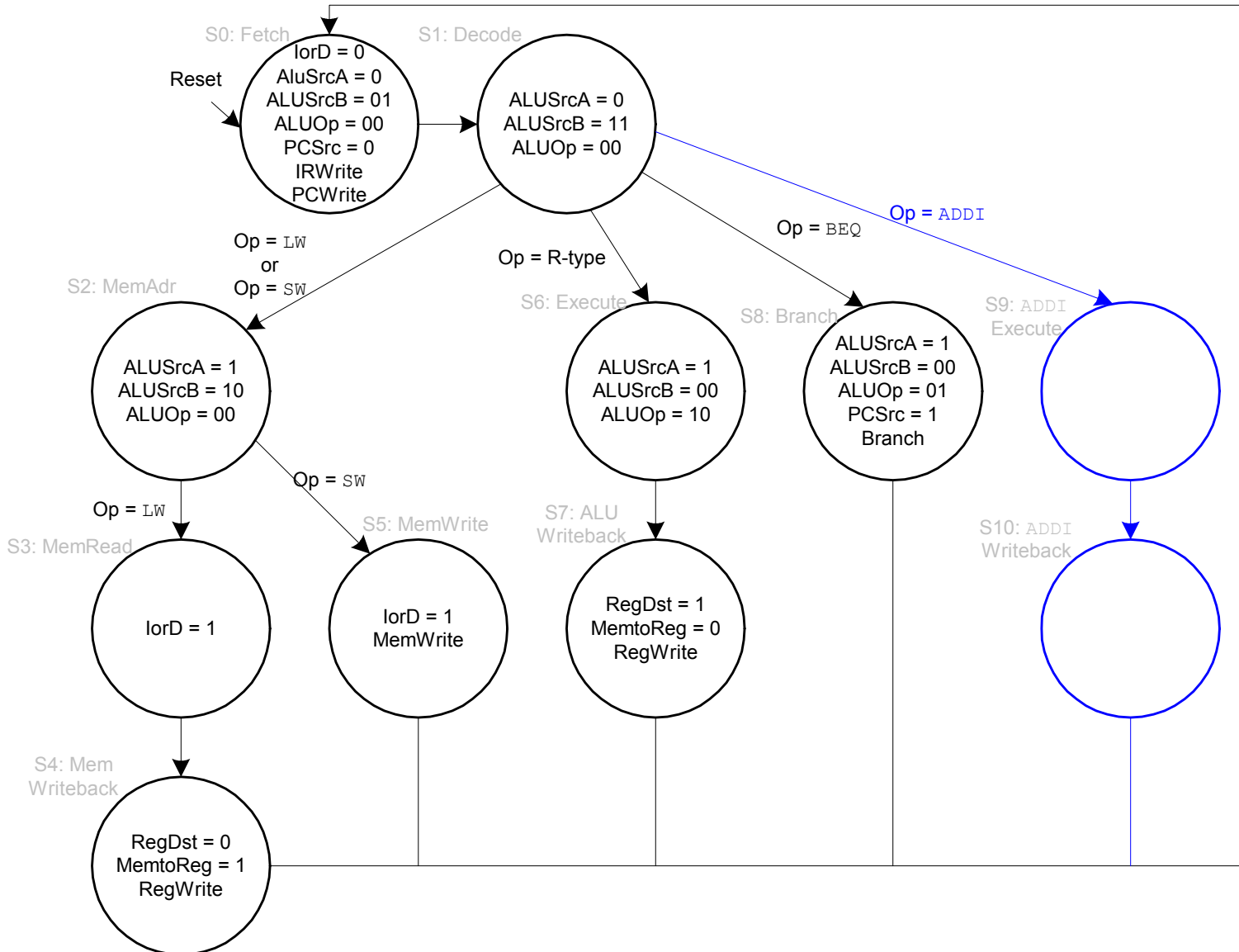


# Main Controller FSM: addi

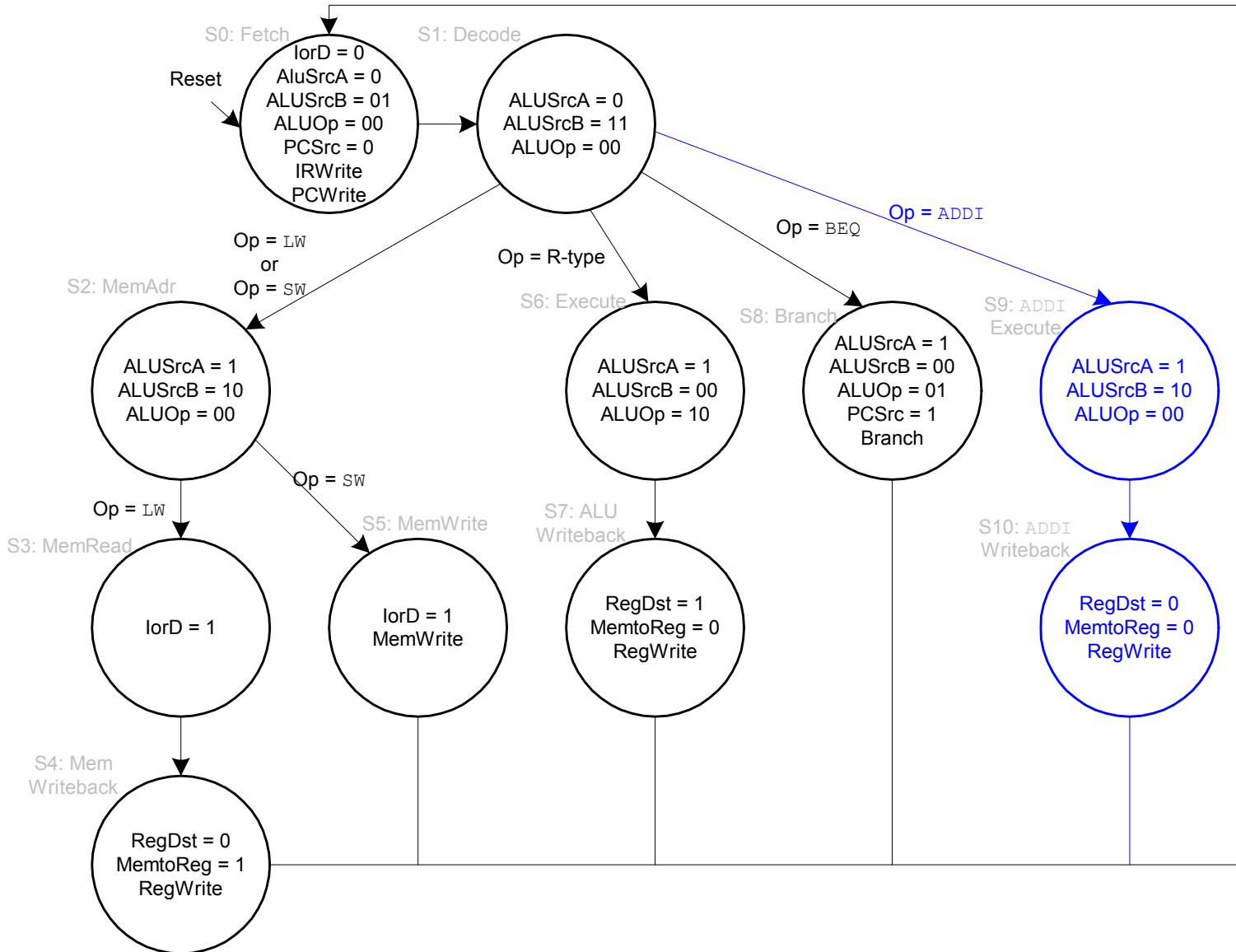


# Extended Functionality: j

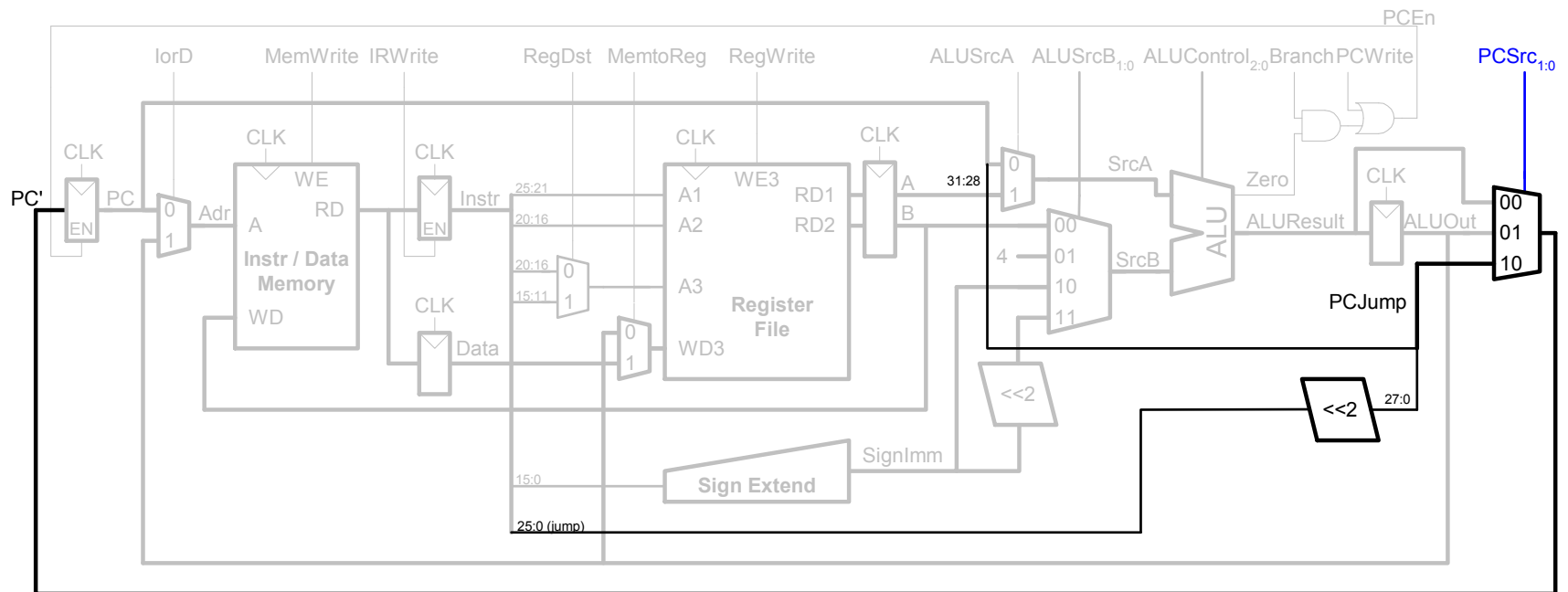

# Control FSM: j

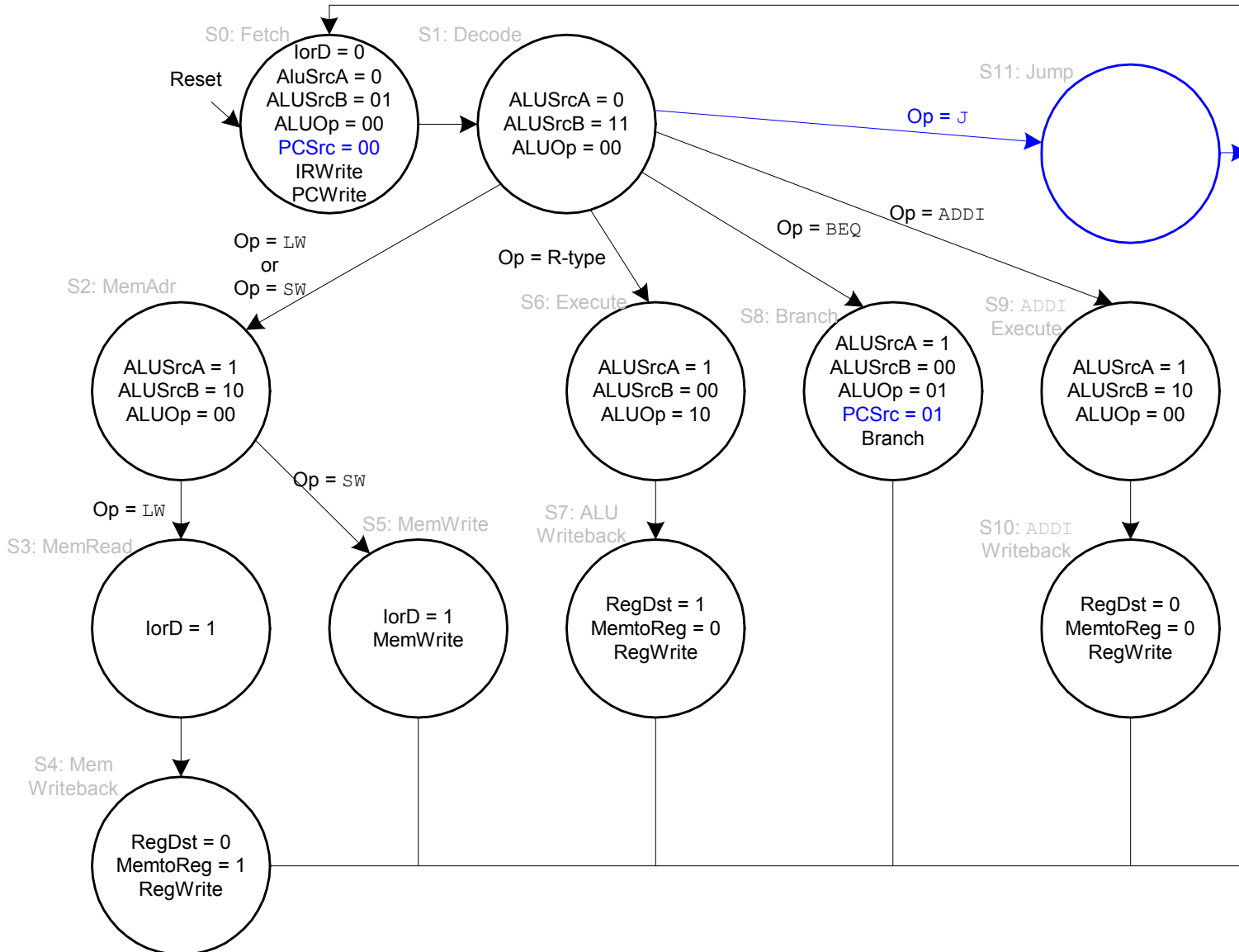

# Control FSM: j

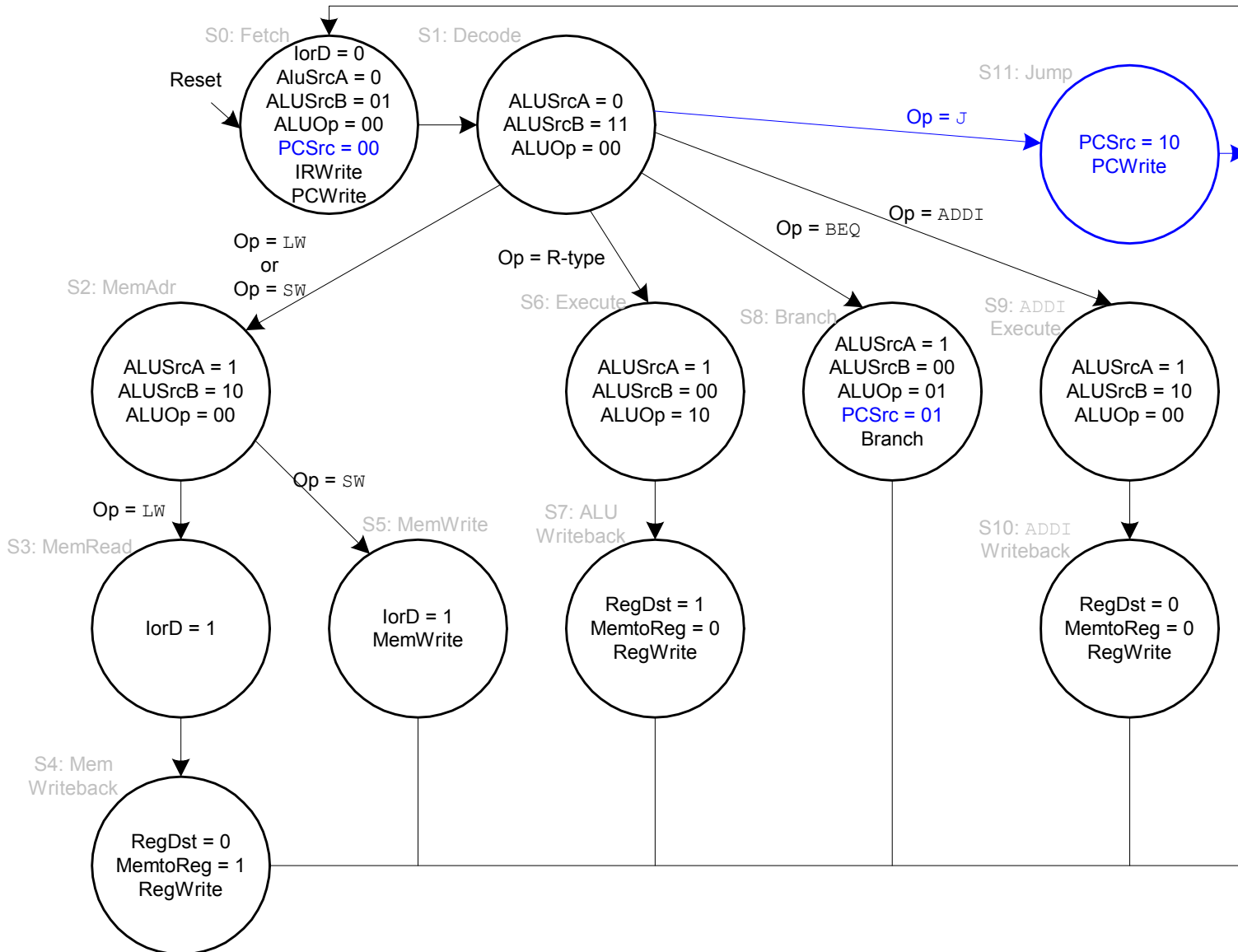

# Summary of Multi-cycle Design

---


- Multi-cycle microarchitecture:
  - + higher clock frequency
  - + simpler instructions run faster
  - + reuse expensive hardware across multiple cycles
- **Need to store the intermediate results** at the end of each clock cycle
  - Hardware overhead for registers
  - Register setup/hold overhead paid multiple times for an instruction



# Performance Analysis

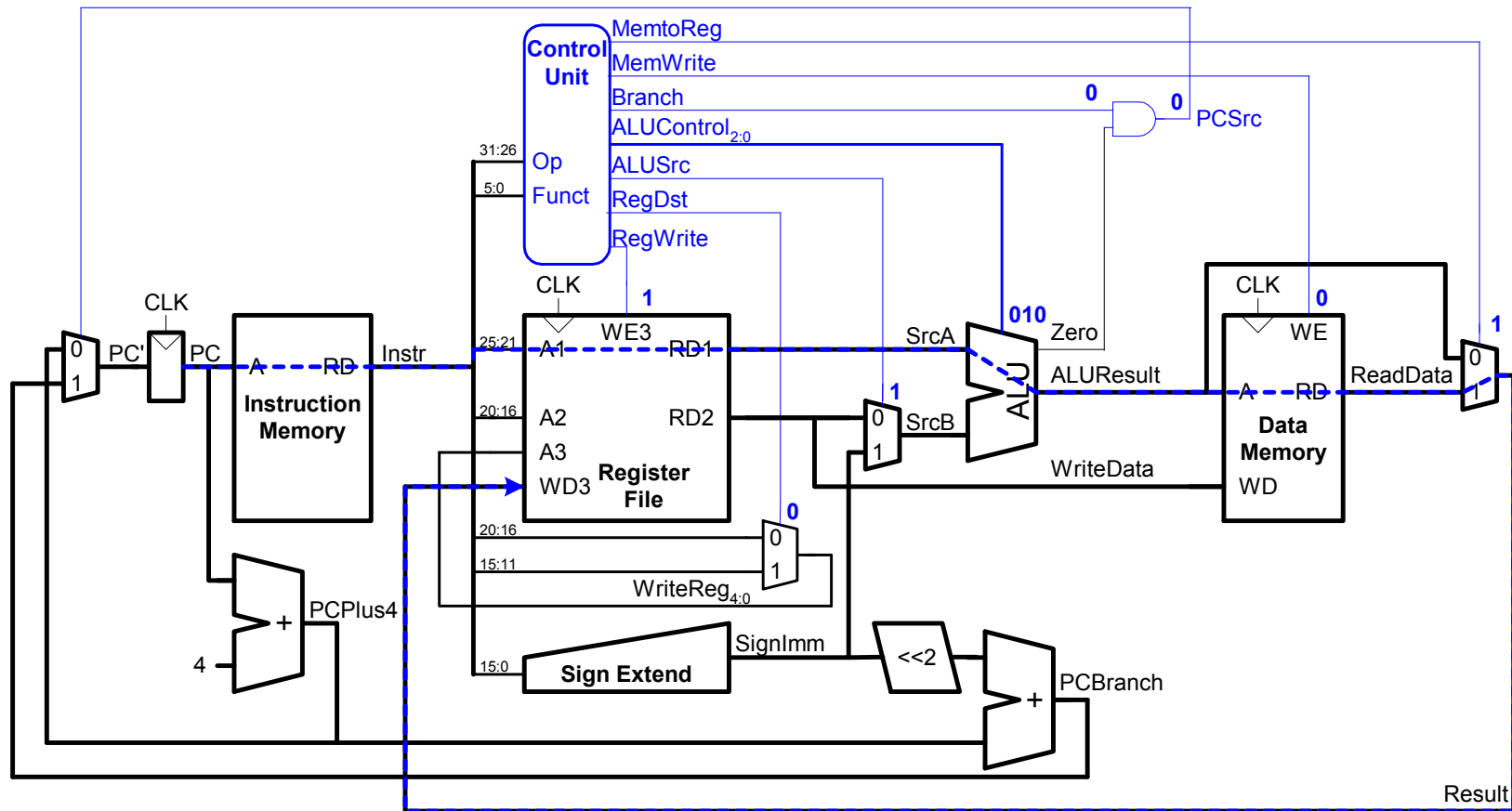
# Single-Cycle Performance

- $T_C$  is limited by the critical path (1w)


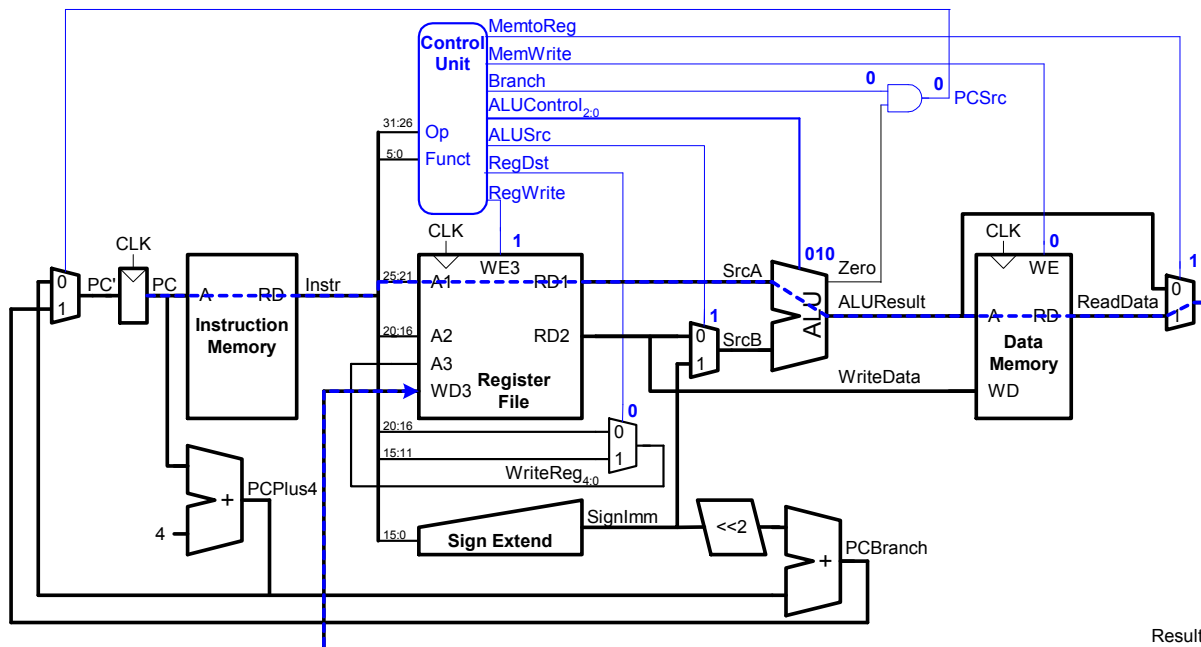
# Single-Cycle Performance

- Single-cycle critical path:
  - $T_c = t_{pcq\_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$
- In most implementations, limiting paths are:
  - memory, ALU, register file.
  - $T_c = t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$



# Single-Cycle Performance Example

---

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$

# Single-Cycle Performance Example

---

- Example:

For a program with 100 billion instructions executing on a single-cycle MIPS processor:

# Single-Cycle Performance Example

---

- Example:

For a program with 100 billion instructions executing on a single-cycle MIPS processor:

$$\begin{aligned}\textbf{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$

# Multi-Cycle Performance: CPI

---


- Instructions take different number of cycles:
  - 3 cycles: `beq, j`
  - 4 cycles: `R-Type, sw, addi`
  - 5 cycles: `lw` **Realistic?**
- CPI is weighted average, e.g. SPECINT2000 benchmark:
  - 25% loads
  - 10% stores
  - 11% branches
  - 2% jumps
  - 52% R-type
- *Average CPI* =  $(0.11 + 0.02) 3 + (0.52 + 0.10) 4 + (0.25) 5$   
= 4.12



# Multi-Cycle Performance: Cycle Time

- Multi-cycle critical path:


$$T_c =$$

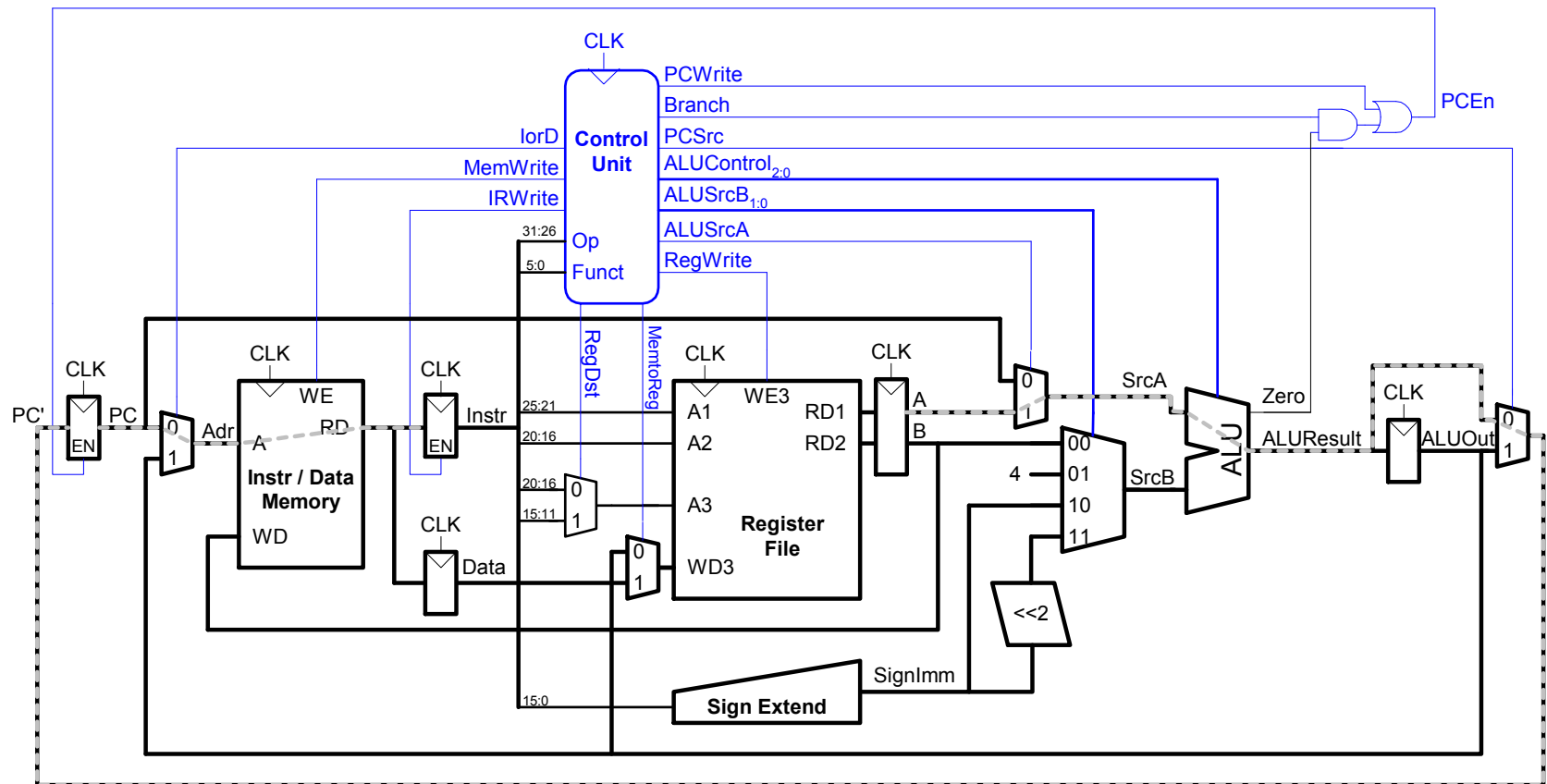
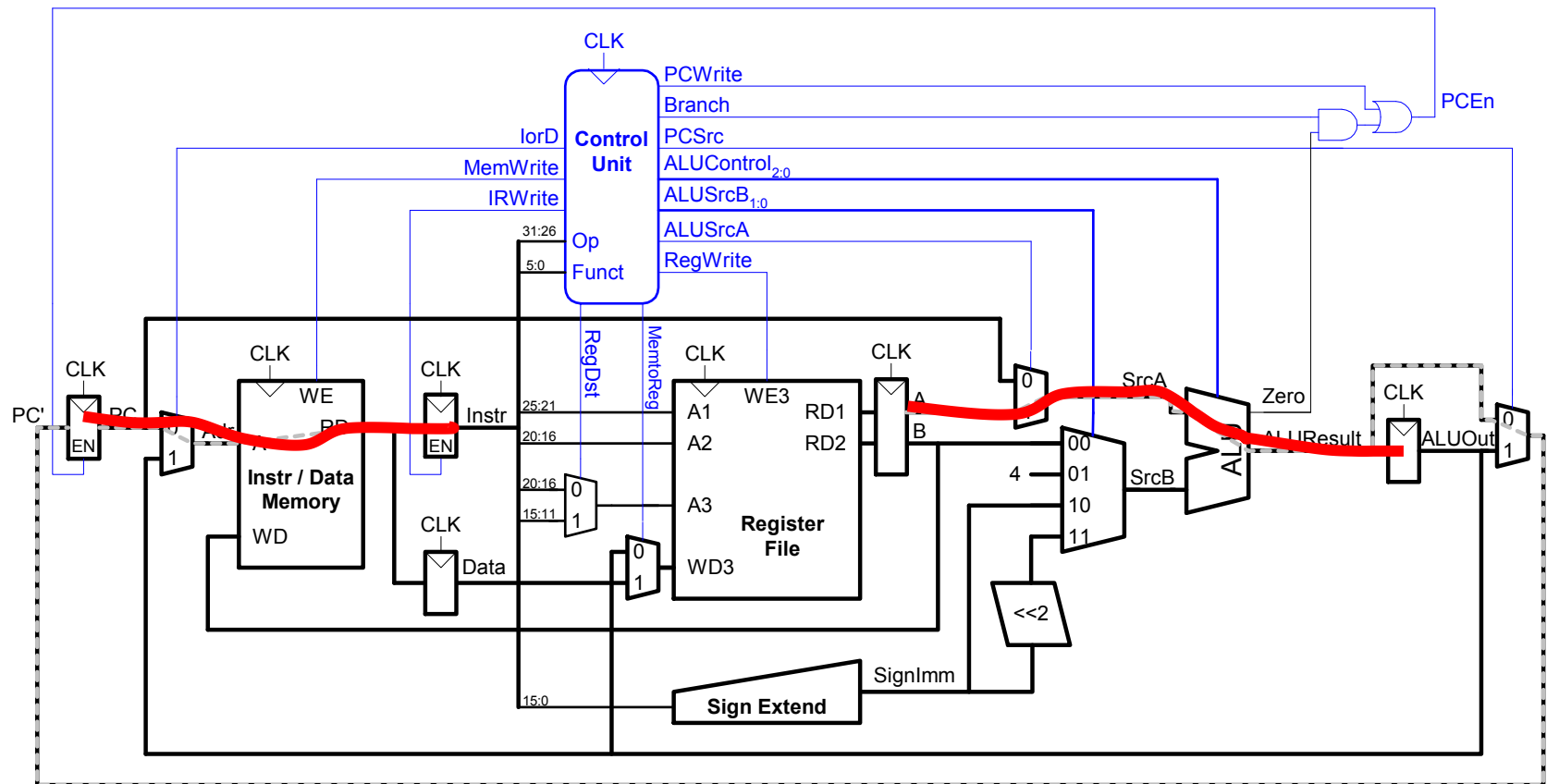
# Multi-Cycle Performance: Cycle Time

- Multi-cycle critical path:

$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



# Multi-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20


$$\begin{aligned}T_c &= t_{pcq\_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\&= [30 + 25 + 250 + 20] \text{ ps} \\&= 325 \text{ ps}\end{aligned}$$

# Multi-Cycle Performance Example


---

- For a program with 100 billion instructions executing on a multi-cycle MIPS processor
  - $CPI = 4.12$
  - $T_c = 325 \text{ ps}$
- *Execution Time* =  $(\# \text{ instructions}) \times CPI \times T_c$   
=  $(100 \times 10^9)(4.12)(325 \times 10^{-12})$   
= 133.9 seconds
- This is slower than the single-cycle processor (92.5 seconds). Why?
- Did we break the stages in a balanced manner?
- Overhead of register setup/hold paid many times
- How would the results change with different assumptions on memory latency and instruction mix?


# Review: Single-Cycle MIPS Processor

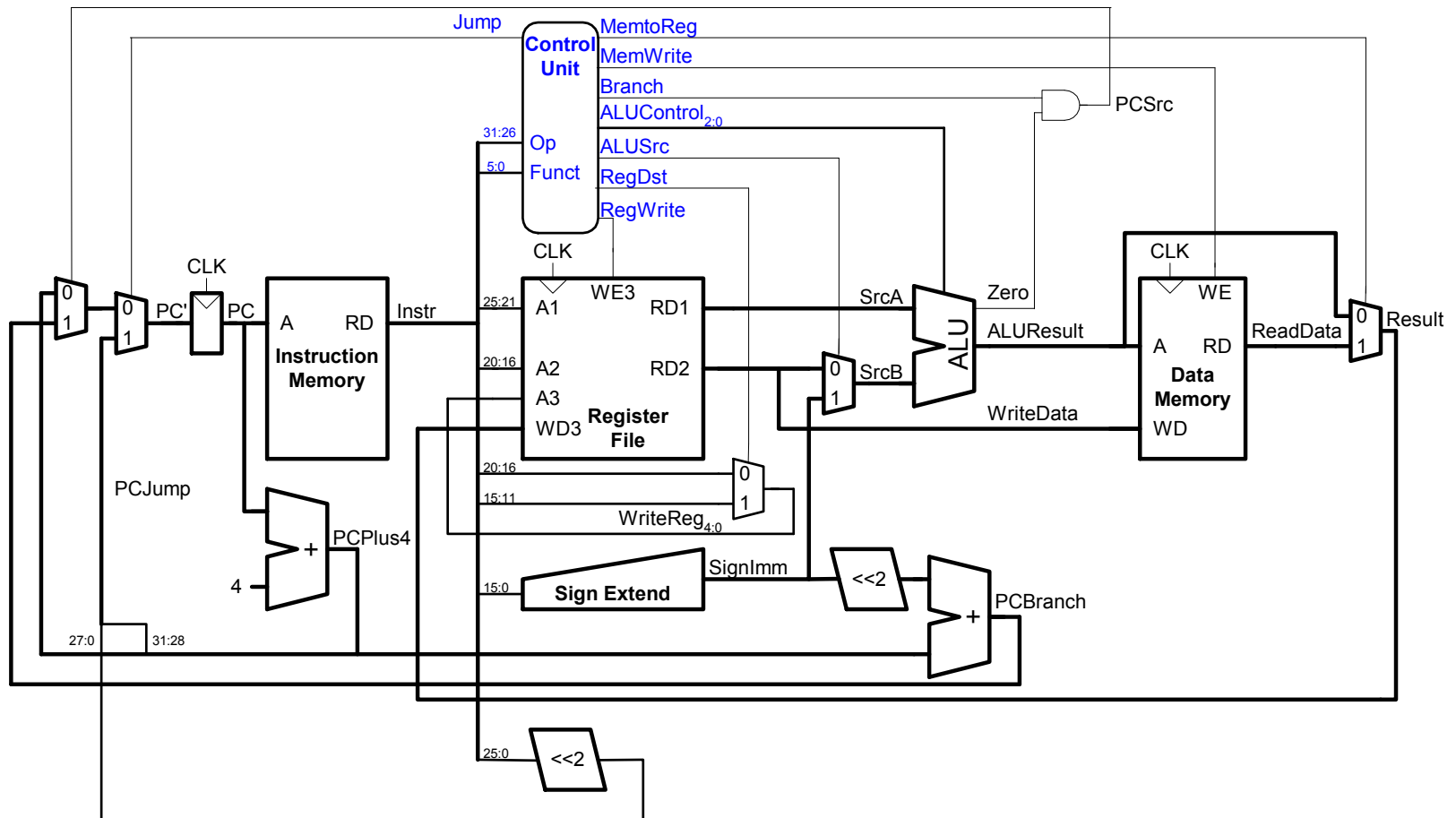

# Review: Multi-Cycle MIPS Processor

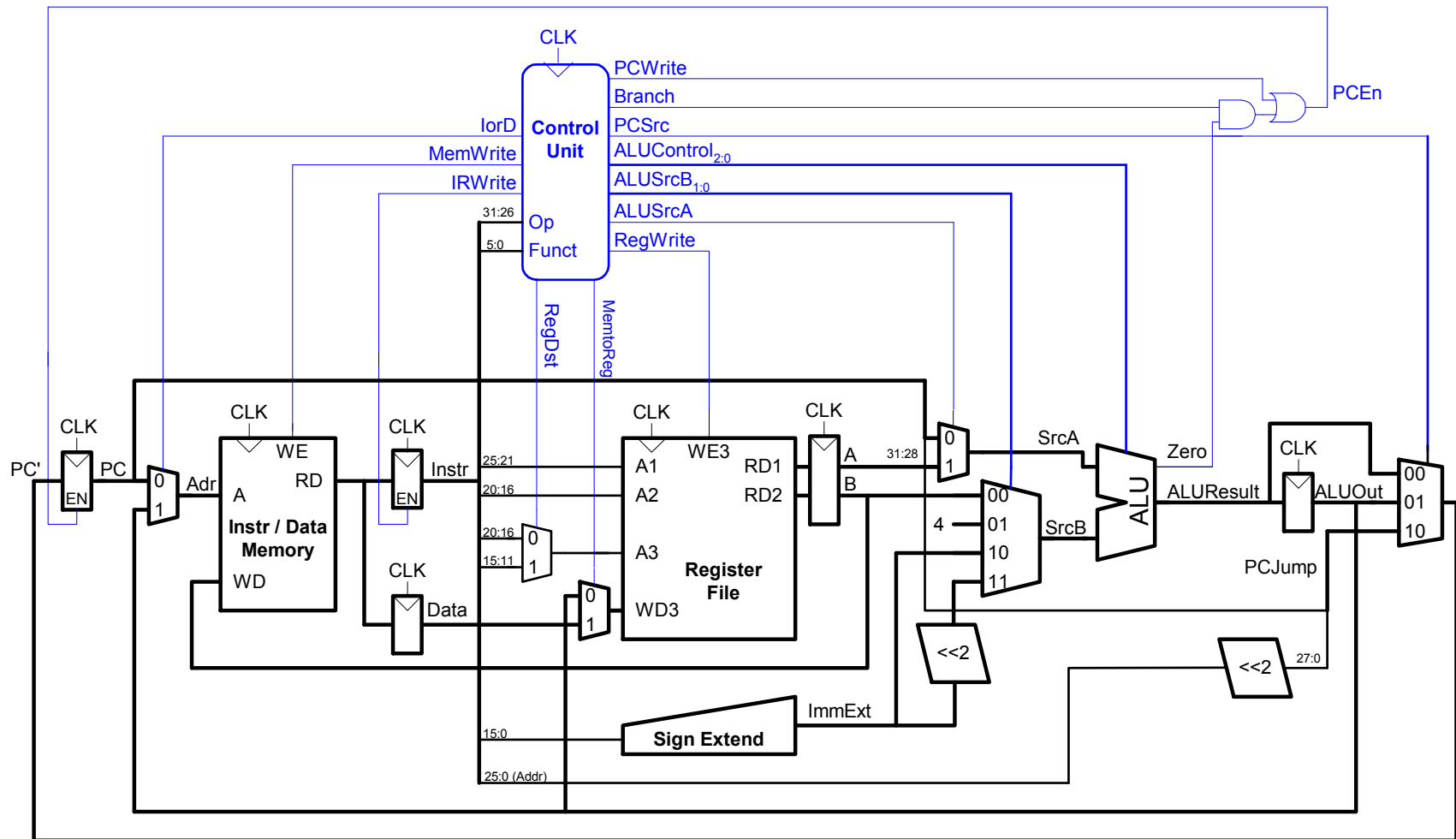

# Review: Multi-Cycle MIPS FSM

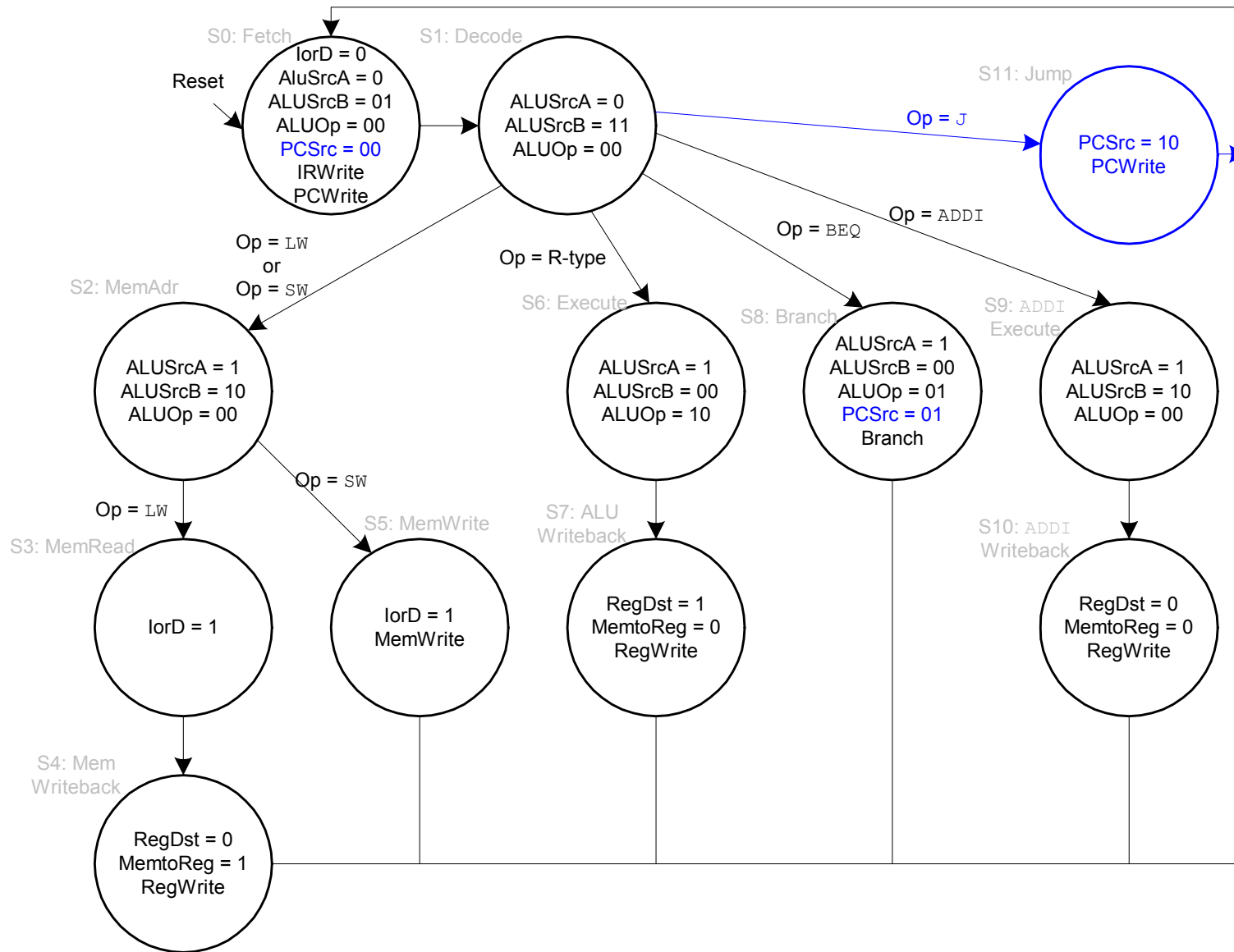

**What is the  
shortcoming of  
this design?**

**What does  
this design  
assume  
about memory?**


# What If Memory Takes $>$ One Cycle?

---

- Stay in the same “memory access” state until memory returns the data
- “Memory Ready?” bit is an input to the control logic that determines the next state



# Foreshadowing: Pipelined Datapath

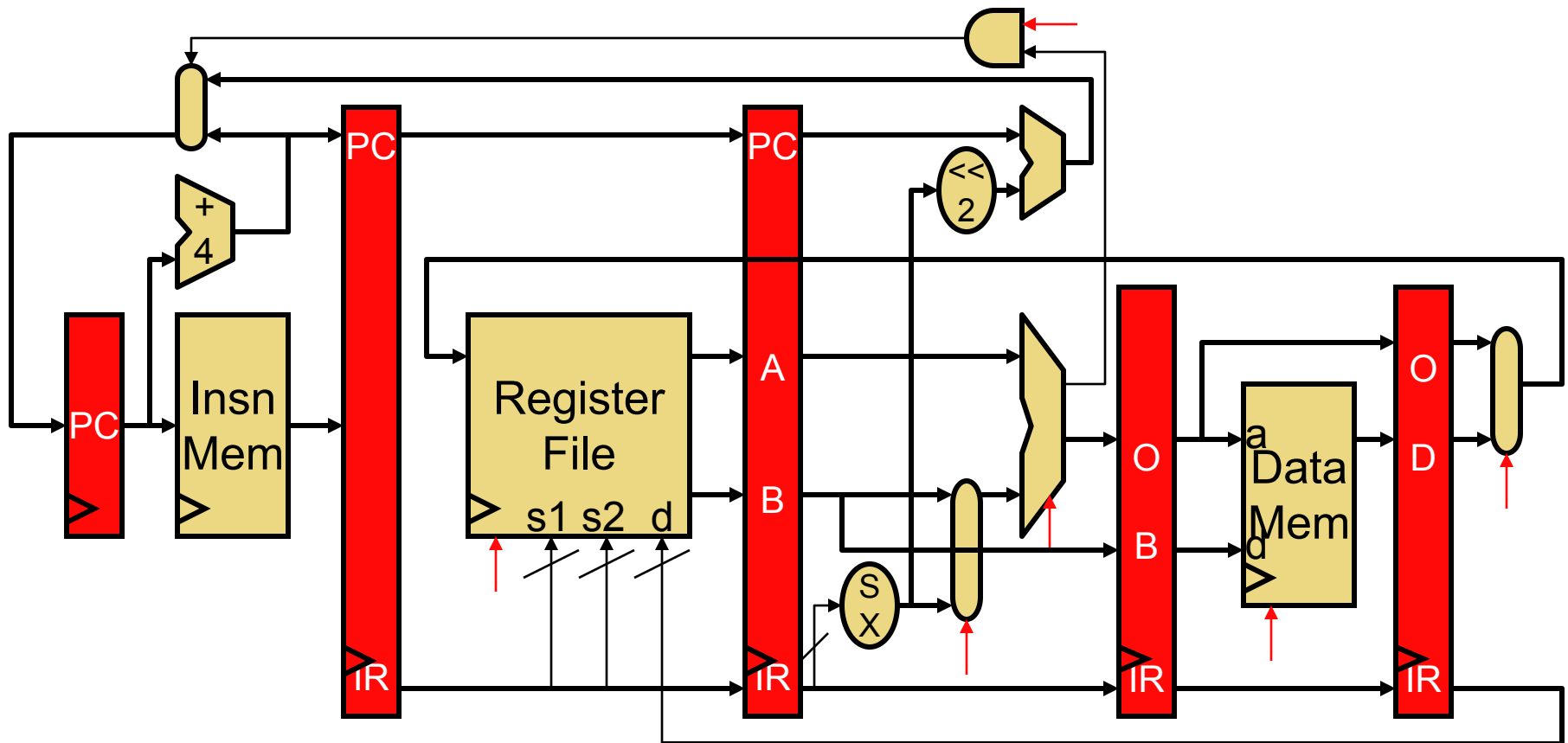

- Split datapath into multiple stages
  - Assembly line analogy
  - 5 stages results in up to 5x clock & performance improvement